
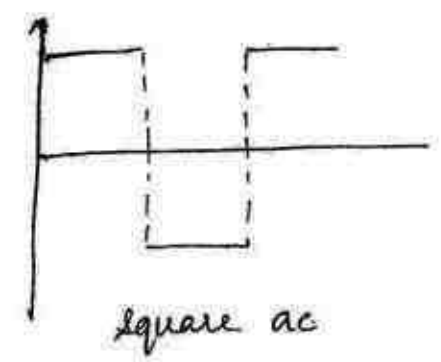
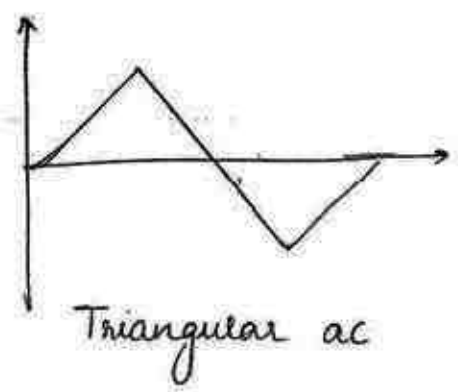
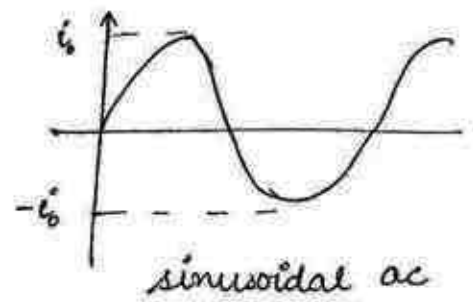


$V_{rms} = \frac{V_0}{\sqrt{2}}$

ALTERNATING CURRENT

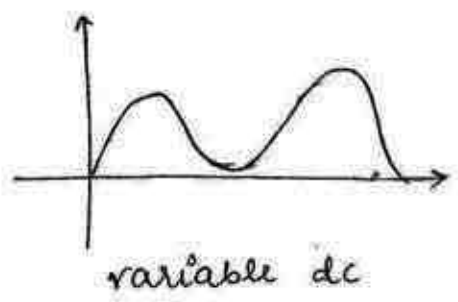- A current in a circuit is called A.C. if -
- > It changes its dirⁿ after every half cycle
 - > Its amplitude remains constant with time



Different values in ac:

for $i = i_0 \sin \omega t$
 $v = v_0 \sin \omega t$

- i) instantaneous value
 $i =$ instantaneous value
- ii) ~~the~~ max / Peak value:
 $i_0 =$ max value

no instrument is designed on this concept coz it gives zero value
 ☹️

iii) average value of ac
 average value of any current for any interval is given by
 $0 \quad 1 \quad 2 \quad -2 \quad -1 \quad 0 \quad ; \quad \therefore \text{avg} = 0$

☺️ it gives max value ☺️

$$i_{avg} = \bar{i} = \langle i \rangle = \frac{\int_{t_1}^{t_2} i dt}{t_2 - t_1} = \frac{\text{area}}{\text{interval}}$$

a) avg. value for full cycle:  ∴ $\frac{\text{area}}{\text{interval}} = 0$

$$\bar{i}_T = \bar{i}_0 \overline{\sin \omega t} \quad \boxed{\bar{i}_T = 0}$$

b) avg value for half cycle: $\frac{T}{2}$   area = 0

$$T = \frac{\int_0^{T/2} i dt}{\frac{T}{2} - 0} = \frac{2i_0 \int_0^{T/2} \sin \omega t dt}{T}$$

$$= -\frac{2i_0}{\omega T} \left(\frac{\cos \omega t}{\omega} \right)_0^{T/2} = -\frac{2i_0}{\omega T} (\cos \frac{\omega T}{2} - \cos 0)$$

$$= -\frac{2i_0}{2\pi} (\cos \pi - \cos 0) \quad \{ \omega T = 2\pi \}$$

$$\therefore \boxed{\bar{i} = \frac{2i_0}{\pi}} \Rightarrow I_{dc} \text{ for full wave rectifier in electronics} \quad \bar{i} = 0.636 i_0$$

c) rms value / apparent value / virtual value / effective:

rms value of ac for any interval is given by

$$i_{rms} = \sqrt{\overline{i^2}} = \sqrt{\frac{\int_{t_1}^{t_2} i^2 dt}{t_2 - t_1}}$$

square
↓
mean
↓
root

$$\text{So, } \sqrt{\overline{i^2}} = \sqrt{\frac{\int_0^T i_0^2 \sin^2 \omega t dt}{T - 0}}$$

$$= i_0 \sqrt{\frac{T \int_0^T \left(\frac{1 - \cos 2\omega t}{2} \right) dt}{T}} \quad \left\{ \begin{array}{l} \because \cos 2\omega t = 1 - 2\sin^2 \omega t \\ \therefore \sin^2 \omega t = \frac{1 - \cos 2\omega t}{2} \end{array} \right.$$

* so all the ac instrument measures rms value of ac

Q) A current in circuit is given by 2A, 50Hz then find

i) after what time, current will attain its max and rms value

ii) max, avg, rms, and instantaneous value of given current.

i) a) $i = i_0 \sin \omega t$

$$i_0 = i_0 \sin \omega t$$

$$\therefore \sin \omega t = \sin \frac{\pi}{2}$$

$$\therefore \omega t = \frac{\pi}{2}$$

$$2\pi f t = \frac{\pi}{2}$$

$$\therefore t = \frac{1}{4f} = \frac{1}{4 \times 50} = \frac{1}{200} \text{ sec}$$

$$2a) \quad \frac{i_0}{\sqrt{2}} = i_0 \sin \omega t \quad \left\{ i_{\text{rms}} \right\}$$

$$\sin \frac{\pi}{4} = \sin \omega t$$

$$\therefore \frac{\pi}{4} = \omega t$$

$$\frac{\pi}{4} = 2\pi f t$$

$$\therefore t = \frac{1}{8f} = \frac{1}{400} \text{ sec}$$

$$i) \Rightarrow i_{\text{rms}} = 2A \quad [i_{\text{rms}}]$$

$$\Rightarrow i_0 = \sqrt{2} i_{\text{rms}} = 2\sqrt{2} \quad [i_{\text{max}}] \quad \left\{ \because i_{\text{rms}} = \frac{i_0}{\sqrt{2}} \right\}$$

$$\Rightarrow i = i_0 \sin(2\pi f t) = 2\sqrt{2} \sin(100\pi t) \quad [i_{\text{instant}}]$$

$$\therefore i = i_0 \sin \omega t$$

$$\Rightarrow \overline{i} = \overline{i_0 \sin \omega t} = 0 \quad [i_{\text{avg}}]$$

$$\ast \text{MRT} \left\{ \begin{array}{l} \overline{\sin \theta} = \overline{\cos \theta} = 0 \\ \overline{\sin^2 \theta} = \overline{\cos^2 \theta} = \frac{1}{2} \\ \omega T = 2\pi \end{array} \right.$$

$$\ast \left\{ \begin{array}{l} 2 \sin \theta \cos \theta = \sin 2\theta \\ \sin^2 \theta + \cos^2 \theta = 1 \end{array} \right.$$

$$\cos \theta = \sin\left(\theta + \frac{\pi}{2}\right) = \sin\left(\theta - \frac{\pi}{2}\right)$$

Q) If ac voltage is given by $V = 622 \sin(50\pi t) \cos(50\pi t)$ then find max value, rms value and average value for ~~the~~ half cycle of voltage.

$$V = 311 [2 \sin(50\pi t) \cos(50\pi t)]$$

$$= 311 \sin(100\pi t) \text{ volt} \Rightarrow \text{eq. ghar ghar ki } iP$$

$$V_0 = \boxed{311}, \quad V_{\text{rms}} = \frac{V_0}{\sqrt{2}} = \frac{311}{\sqrt{2}} = \boxed{220 \text{ volt}}$$

$$\overline{V_{T/2}} = \left(\frac{2V_0}{\pi} \right) = \boxed{198 \text{ volt}}$$

Q) A 3A dc is superimposed on $4 \sin \omega t$ ac, then find max, avg, and rms values of the resultant current

$$\Rightarrow \overset{i}{i}_{\text{max}} = i_{\text{ac}} + i_{\text{dc}} \\ = 4 \sin \omega t + 3 = 4 + 3 = \boxed{7A}$$

$$\Rightarrow \overline{i_{\text{avg}}} = \overline{3 + 4 \sin \omega t} \\ = 3 + 4 \times 0 = \boxed{3A}$$

$$\Rightarrow \overset{i}{i}_{\text{rms}} \Rightarrow \because i = 3 + 4 \sin \omega t \\ \therefore \overline{i^2} = \overline{9 + 16 \sin^2 \omega t + 24 \sin \omega t} \\ \overline{i^2} = 9 + 16 \times \frac{1+0}{2} = 17$$

$$\therefore \overset{i}{i}_{\text{rms}} = \sqrt{\overline{i^2}} = \boxed{\sqrt{17}}$$

Q) An ac of $3 \sin \omega t$ is superimposed on another of $4 \cos \omega t$. Then find peak, ~~max~~^{avg}, rms, of resultant.

$$\rightarrow \therefore i = 3 \sin \omega t + 4 \cos \omega t$$

$$I_0 = \sqrt{3^2 + 4^2 + 2 \times 3 \times 4 \cos \frac{\pi}{2}} = \boxed{5A = I_{\max}}$$

$$\rightarrow \text{max } \overline{i} = \overline{3 \sin \omega t} + \overline{4 \cos \omega t} = \boxed{0 = I_{\text{avg}}}$$



$$\begin{aligned} \rightarrow \overline{i^2} &= \overline{9 \sin^2 \omega t} + \overline{16 \cos^2 \omega t} + \overline{24 \sin \omega t \cos \omega t} \\ &= 9 \times \frac{1}{2} + 16 \times \frac{1}{2} + 0 = \frac{25}{2} \end{aligned}$$

$$\therefore \sqrt{\overline{i^2}} = \boxed{\frac{5}{\sqrt{2}} = I_{\text{rms}}}$$



Phasor Quantities :

These are the quantities which behaves like an vector due to phase angle also called rotating vectors



$$i) \quad i = i_0 \sin \omega t$$

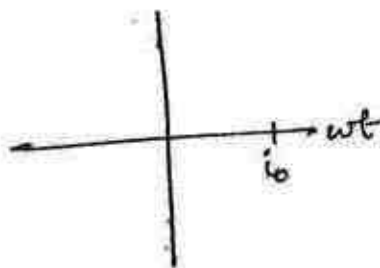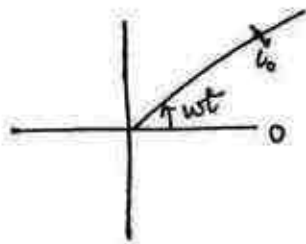
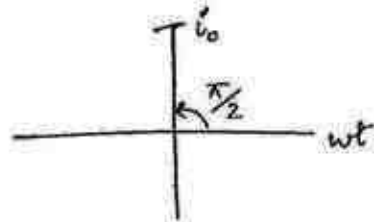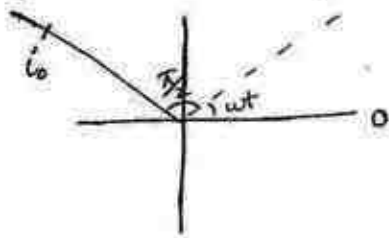
$$ii) i = i_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$



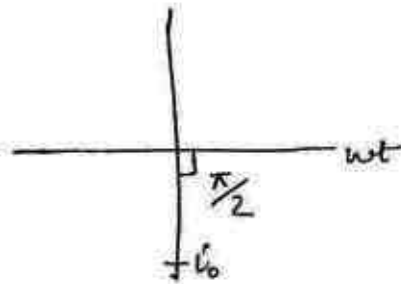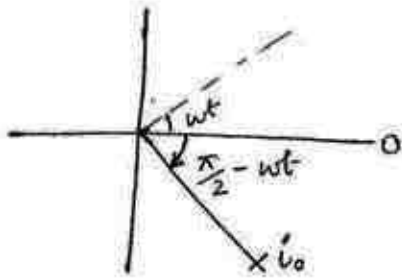
$$iii) i = i_0 \sin\left(\omega t - \frac{\pi}{2}\right)$$



different element in ac circuit :

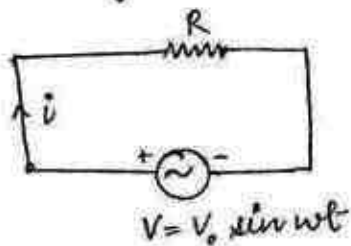i) If only resistance (R) is connected in circuit.



By KVL,

$$-iR + V = 0$$

$$\therefore V_0 \sin \omega t = iR$$

$$\therefore i = \frac{V_0}{R} \sin \omega t$$

$$\therefore \boxed{i = i_0 \sin \omega t}$$


$$\therefore V = V_0 \sin \omega t \text{ and } i = i_0 \sin \omega t$$

> Phase diffⁿ b/w V and i



$$\text{Phase diff}^n \phi = \omega t - \omega t = 0 \therefore \boxed{\phi = 0}$$

so across the resistance, V and i are in same phase

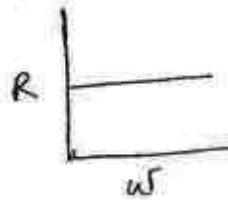
as $R \propto \omega^0$, so behaviour of Resistance is same in ac as well as dc.



→ Phasor diagram:

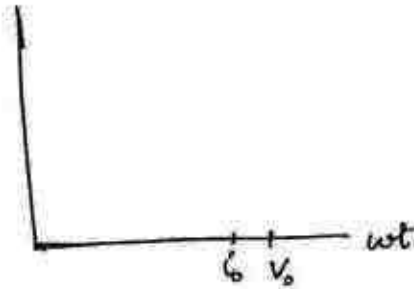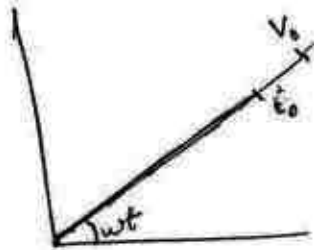

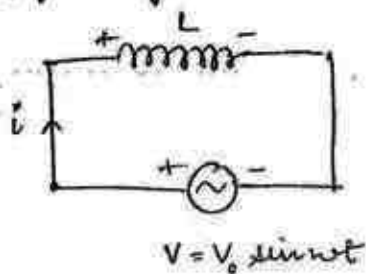ii) If only inductor is connected in circuit



By KVL,

$$-V_L + V = 0$$

$$L \frac{di}{dt} = V_0 \sin \omega t$$

definite integral \neq $\therefore \int di = \frac{V_0}{L} \int \sin \omega t dt$
 \therefore at $t=0$, $i \neq 0$ (eq unknown)

$$i = \frac{V_0}{L} \left(\frac{-\cos \omega t}{\omega} \right) + C$$

here C must be 0 cz there will be no dc component.

$$i = \frac{V_0}{\omega L} - \sin \left(\frac{\pi}{2} - \omega t \right) \quad \because \cos \theta = \sin \left(\theta + \frac{\pi}{2} \right) = -\sin \left(\frac{\pi}{2} - \theta \right) = \sin \left(\theta - \frac{\pi}{2} \right)$$

$$\therefore \boxed{i = \frac{V_0}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)}$$

$$\boxed{i = \frac{V_0}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)}$$

$$\therefore \boxed{X_L = \omega L}$$



> Phase difference $\phi = \omega t - (\omega t - \frac{\pi}{2}) = +\frac{\pi}{2}$

So, voltage leads the current by a phase angle $+\frac{\pi}{2}$ in an inductor

> $X_L =$ Inductive reactance

It represents the resistance offered by the inductor due to its self inductance.

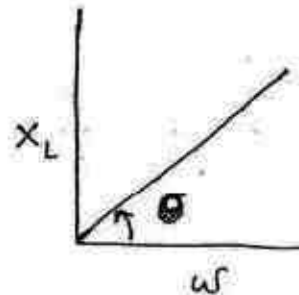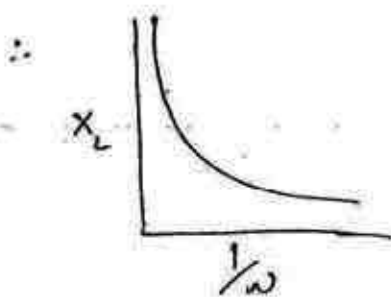$X_L = \omega L$ $\therefore X_L = 2\pi f L$ $\therefore X_L \propto \omega$ ni $X_L \propto L$





slope = $\frac{X_L}{\omega} = L$


> ~~Behaviour of inductor~~ inductor dc ko jane dega if
in dc: $\omega = 0 \therefore X_L = 0 \therefore$ Behaviour \rightarrow connecting wire

in ac: $X_L \propto \omega \therefore \omega \uparrow X_L \uparrow i \downarrow$
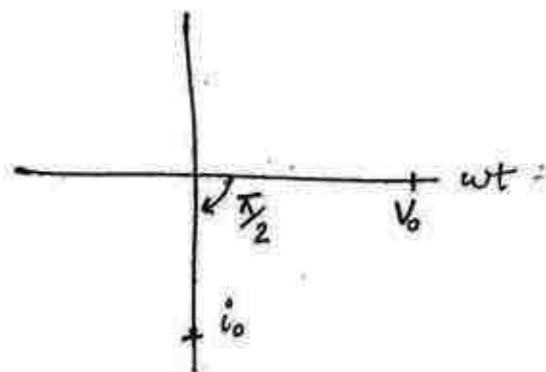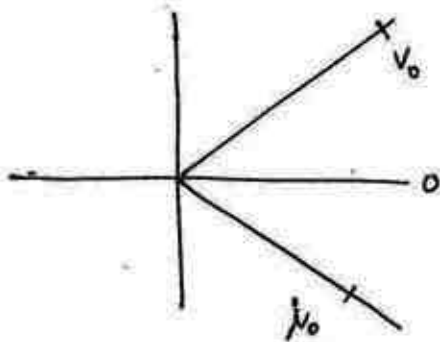
> $V = V_0 \sin \omega t$ and $i = i_0 \sin (\omega t - \frac{\pi}{2})$



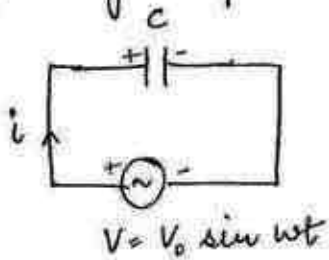iii) If only capacitor is connected in circuit



current in circuit

By KVL,

$$-V_c + V = 0$$

$$\frac{q}{C} = V_0 \sin \omega t$$

$$\therefore q = CV_0 \sin \omega t$$

$$\therefore \frac{dq}{dt} = CV_0 \omega \cos \omega t$$

$$\therefore i = \frac{V_0}{\left[\frac{1}{C\omega} \right]} \sin \left(\omega t + \frac{\pi}{2} \right)$$

$$\therefore i = \frac{V_0}{[X_c]} \sin \left(\omega t + \frac{\pi}{2} \right)$$

$$\therefore X_c = \frac{1}{C\omega}$$

> Phase difference:

$$\phi = \omega t - \left(\omega t + \frac{\pi}{2} \right) = -\frac{\pi}{2}$$

\therefore Voltage lags behind the current by a phase angle $\frac{\pi}{2}$
capacitor \rightarrow current \rightarrow current \therefore In capacitor, current leads by $\frac{\pi}{2}$

> $X_c =$ capacitive reactance

It represents the resistance offered by the capacitor as existing charge always repels upcoming charge.

$$X_c = \frac{1}{\omega C}$$

$$X_c = \frac{1}{2\pi f C}$$

$$\therefore X_c \propto \frac{1}{\omega}$$

X_c

X_c

Behaviour of capacitor.



In dc $\omega = 0 \therefore X_c = \infty \therefore i = 0$

In ac $X_c \propto \frac{1}{\omega} \therefore \omega \uparrow X_c \downarrow \therefore i \uparrow$

So, inductor opposes high frequency ac. but

capacitor blocks dc
effect of dc $\begin{cases} \text{on capacitor} \Rightarrow \text{blocks} \\ \text{on inductor} \Rightarrow \text{no effect} \end{cases}$

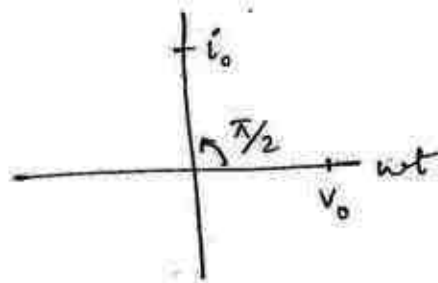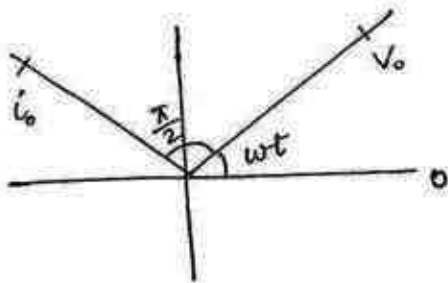$V = V_0 \sin \omega t \quad i = i_0 \sin \left(\omega t + \frac{\pi}{2} \right)$



Q) An inductor of 1 H is connected across ac source of 200 V, $100/\pi$ Hz. Find current through inductor.

$$i = \frac{V_0}{X_L} = \frac{V_0}{\omega L} = \frac{V_0}{2\pi f L}$$

$$= \frac{200}{2\pi \frac{100}{\pi} \times 1} = 1 \text{ A}$$

Q) An ac voltage is given by $V = 100\sqrt{2} \sin(100t)$ volt. Then find current through the following element

- i) Resistance of 10 Ω
- ii) Inductance of 10 H and
- iii) capacitance of 10 μF


$$i) i = \frac{V_{rms}}{R} = \left(\frac{100\sqrt{2}}{\sqrt{2}} \right) 10 = 10 \text{ A}$$

$$ii) i = \frac{V_{rms}}{\omega L} = \frac{100}{100 \times 10} = 0.1 \text{ A}$$


$$iii) i = \frac{V_{rms}}{\frac{1}{\omega C}} = V_{rms} \omega C = 100 \times 100 \times (10 \times 10^{-6}) = 0.1 \text{ A}$$

Series R-L-C combination

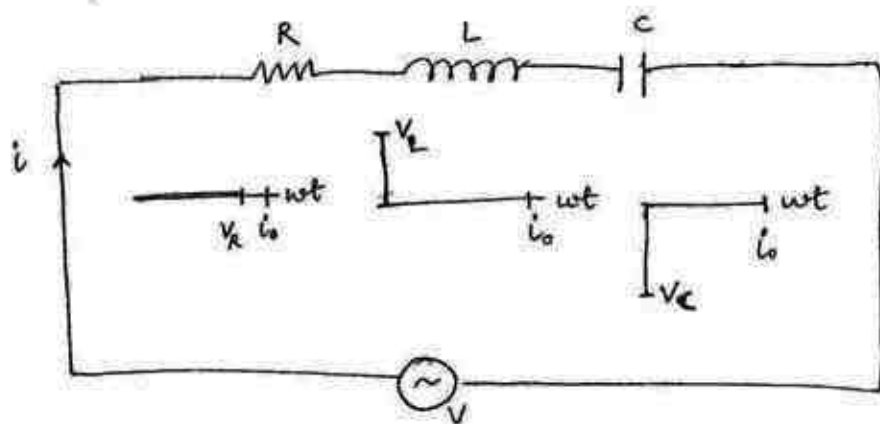Let a resistance R , inductance L , and capacitance C are connected in series, then current through each element. $i = i_0 \sin \omega t$ will remain same.



Phasor diagram

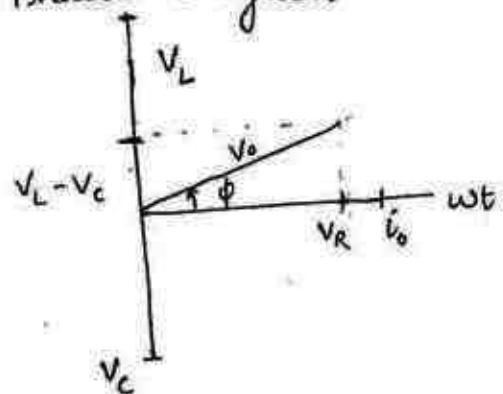


$$V = V_0 \sin(\omega t \pm \phi)$$

$V_L > V_C \quad (+\phi)$
 $V_L < V_C \quad (-\phi)$

here,

$$V_0 = \sqrt{V_{0R}^2 + (V_{0L} - V_{0C})^2}$$

> Voltage triangle

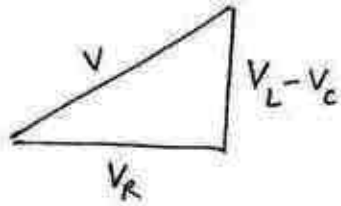

$$\therefore V = \sqrt{V_R^2 + (V_L - V_C)^2} \quad \text{--- (1)}$$

$$\Rightarrow V_R = iR$$

$$V_L = iX_L$$

$$V_C = iX_C$$

$$V = iZ \quad \because Z = \text{impedance}$$


here, impedance represents total resistance offered by all the element in circuit

From eq. (1)

$$iZ = \sqrt{(iR)^2 + (iX_L - iX_C)^2}$$

$$\therefore Z = \sqrt{R^2 + (X_L - X_C)^2}$$

> Impedance triangle

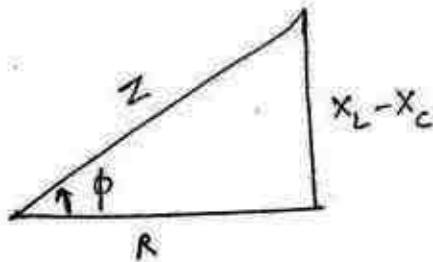


> Phase difference b/w voltage and current.


$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{X_L - X_C}{R}$$

$$\sin \phi = \frac{V_L - V_C}{V} = \frac{X_L - X_C}{Z}$$

** Series R-L circuit

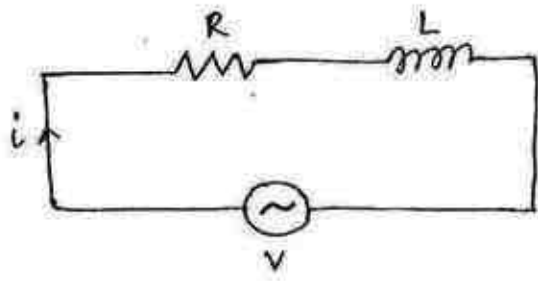


Phasor:

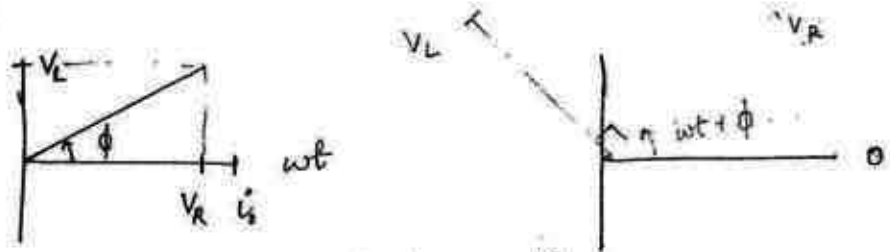

$$V = V_0 \sin(\omega t + \phi)$$


> Voltage triangle

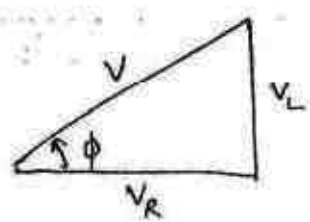

$$V = \sqrt{V_R^2 + V_L^2}$$


> Impedance triangle
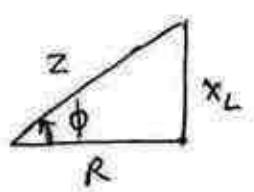
$$iZ = \sqrt{(iR)^2 + (iX_L)^2} \quad \therefore Z = \sqrt{R^2 + X_L^2}$$




$$\tan \phi = \frac{X_L}{R} = \frac{V_L}{V_R}$$


Series R-C circuit

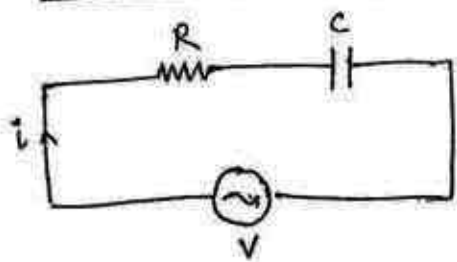

Phasor:

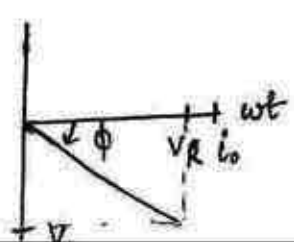

> Voltage Triangle

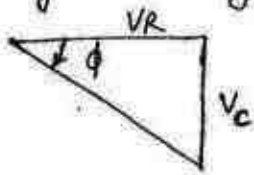


$$\therefore V = \sqrt{V_R^2 + V_C^2}$$

> Impedance Triangle


$$iZ = \sqrt{(iR)^2 + (iX_C)^2}$$

$$\therefore Z = \sqrt{R^2 + X_C^2}$$

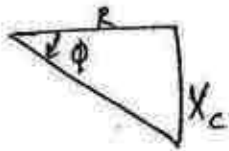


$$\therefore \tan \phi = \frac{V_C}{V_R} = \frac{X_C}{R}$$

Series L-C circuit

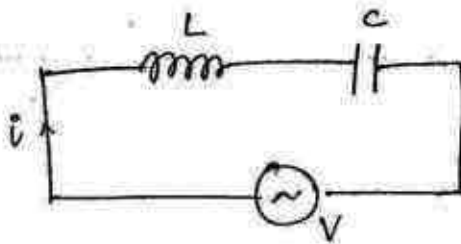

Phasor:

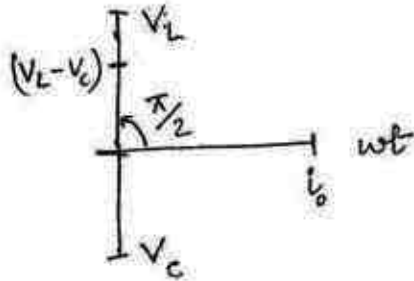

$$\therefore V = V_0 \sin \omega t \pm \frac{\pi}{2}$$

$$V_L > V_C \quad \left(+\frac{\pi}{2}\right)$$

$$V_L < V_C \quad \left(-\frac{\pi}{2}\right)$$

$$V = V_L - V_C$$

$$Z = X_L - X_C$$


$$\phi = \pm \frac{\pi}{2}$$

Q) In series R-L-C circuit, voltages across resistance, inductance and capacitance are 80V, 110V, and 170V, then find applied instantaneous voltage

$$V = \sqrt{80^2 + (110 - 170)^2} = 100 \text{ V} = V_{\text{rms}}$$

$$\therefore V_0 = V_{\text{rms}} \sqrt{2} = 100 \sqrt{2}$$
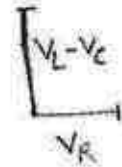
$$\therefore V = V_0 \sin(\omega t \pm \phi) \quad \therefore \tan \phi = \frac{V_L - V_C}{V_R}$$




$$\tan \phi = \frac{110 - 170}{80} = \frac{-3}{4} \quad \therefore \phi = 37^\circ$$

\therefore it's in -ve

$$\therefore V = 100 \sqrt{2} \sin(\omega t - 37^\circ) \quad \therefore V_C > V_L$$

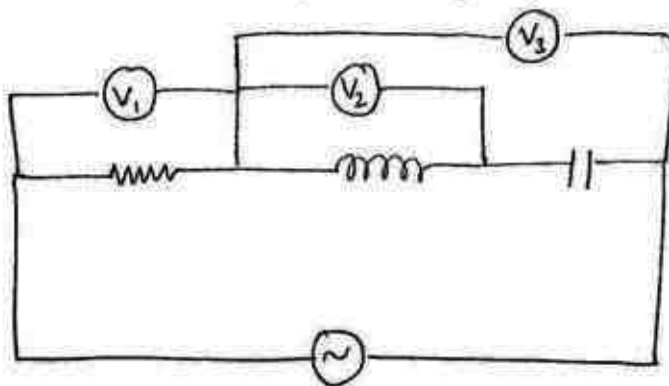Q) In the given diagram, resistance, inductance resistance and capacitance resistance are 30Ω , 100Ω , 60Ω respectively, then find reading of voltmeter V_1, V_2, V_3 if current in the circuit is $i = 2\sqrt{2} \sin(10t)$




$$i_{\text{rms}} = \frac{i_0}{\sqrt{2}} = \frac{2\sqrt{2}}{\sqrt{2}} = 2$$

$$\therefore V_1 = V_R = iR = 2 \times 30 = 60 \text{ V}$$


$$V_2 = iX_L = 2 \times 100 = 200 \text{ V}$$

$$\therefore V_3 = V_2 - V_1 = 200 - 120$$

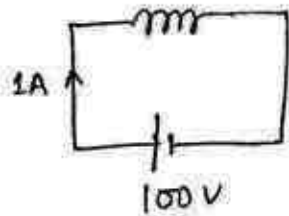Q) A choke coil when connected to dc source of 100V then 1A current flows through it when it is connected to an ac source of 100V, 50 Hz, then 0.5A current flows through. Find its inductance



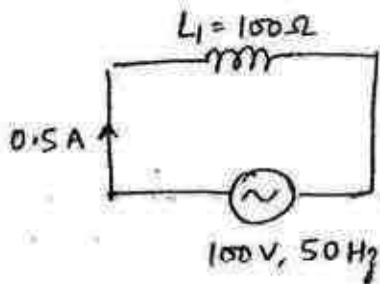
$$R = \frac{V}{i} = \frac{100}{1} = 100 \Omega$$



$$\therefore i = \frac{V}{\sqrt{R^2 + X_L^2}}$$

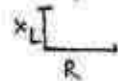$\therefore R$ and X_L are always perpendicular



$$0.5 = \frac{100}{\sqrt{R^2 + X_L^2}}$$

$$\therefore R^2 + X_L^2 = 40,000$$



$$10,000 + X_L^2 = 40,000$$

$$\omega L = X_L = 100\sqrt{3} \quad \Rightarrow \quad 2\pi fL = 100\sqrt{3}$$

($\because f = 50$)

$$\therefore 1000\pi L = \sqrt{3} \times 100; \quad L = \frac{\sqrt{3}}{\pi} \text{ H}$$

L-C oscillations

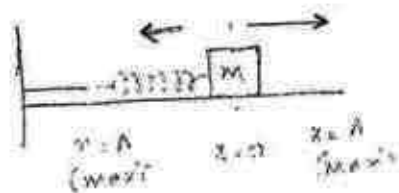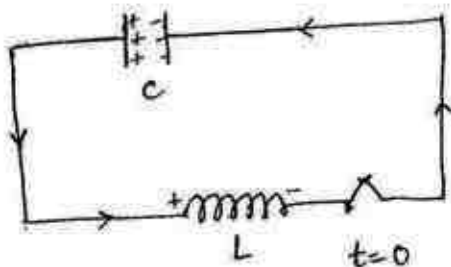

When an charged capacitor is connected to an inductor then due to discharging of capacitor, current i is in circuit which is opposed by the inductor.

The potential energy of the capacitor continuously converted into magnetic energy in the inductor and then magnetic energy starts converting into potential energy in the capacitor. The process continuous to repeat itself considering no heat loss in connecting wire. This phenomenon is called L-C oscillations

Applying KVL for the above circuit

$$-V_L + V_C = 0$$

$$-L \frac{di}{dt} + \frac{q}{C} = 0$$

$$-L \frac{d}{dt} \left(\frac{-dq}{dt} \right) + \frac{q}{C} = 0 \quad (\text{as } q \text{ is decreasing})$$

$$\frac{d^2q}{dt^2} + \frac{1}{LC} q = 0 \quad \text{--- (1) (on dividing by } L)$$

comparing eq (1) with standard equation of SHM

$$\frac{d^2x}{dt^2} + \omega^2 x = 0 \quad \text{--- (2)}$$

then $\boxed{\omega = \frac{1}{\sqrt{LC}}}$ = ω_n = natural frequency of LC oscillati

as solⁿ of eq (2) is $x = A \cos(\omega t + \phi)$

so, solⁿ of eq (1)

$$q = q_0 \cos(\omega t + \phi)$$

initially at $t=0$, $q = q_0$

$$\therefore q_0 = q_0 \cos \phi \quad \therefore \phi = 0$$

so $\boxed{q = q_0 \cos \omega t}$ ~~then~~ $i = \frac{dq}{dt}$

$$\therefore \boxed{i = -q_0 \omega \sin \omega t}$$

$$\therefore U = \frac{1}{2} Li^2$$

$$\therefore \boxed{U = \frac{1}{2} L q_0^2 \omega^2 \sin^2 \omega t}$$

Series R-L-C resonance

when applied frequency in series R-L-C circuit becomes equal to natural frequency of R-L oscillation then, this condition is called resonance.

so, $\omega = \omega_n = \omega_r$ where ω_r = resonating frequency

Regarding series R-L-C resonance

$$\omega_r = \frac{1}{\sqrt{LC}}$$

$$\therefore \omega_r^2 = \frac{1}{LC}$$

$$\therefore \omega_r L = \frac{1}{\omega_r C}$$

$$\therefore \boxed{X_L = X_C}$$

$$iX_L = iX_C \quad \therefore \boxed{V_L = V_C}$$

$$\therefore V = \sqrt{V_R^2 + (V_L - V_C)^2} \quad \therefore \cancel{V \neq P} \quad \boxed{V = V_R} \quad (\because V_L = V_C)$$


$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad \therefore \boxed{Z = R = \text{min}}$$

$$i = \frac{V}{Z_{\text{min}}} \quad \therefore \boxed{i = \frac{V}{R} = \text{max}}$$

$$\tan \phi = \frac{X_L - X_C}{R} = 0 \quad \therefore \phi = 0 \quad (\because X_L = X_C)$$

\therefore V and i are in same phase in resonating condition.

Resonance curve

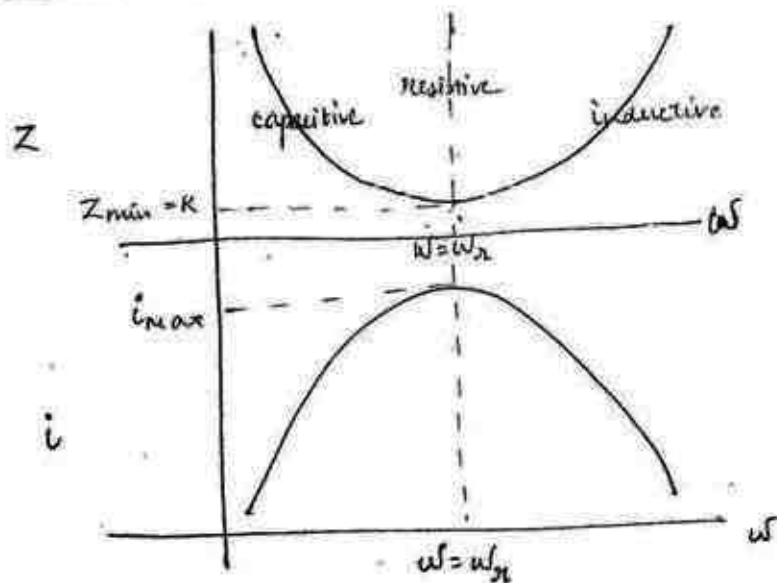


nature of circuit

a) if $\omega < \omega_r \rightarrow$ capacitive

b) if $\omega = \omega_r \rightarrow$ resistive

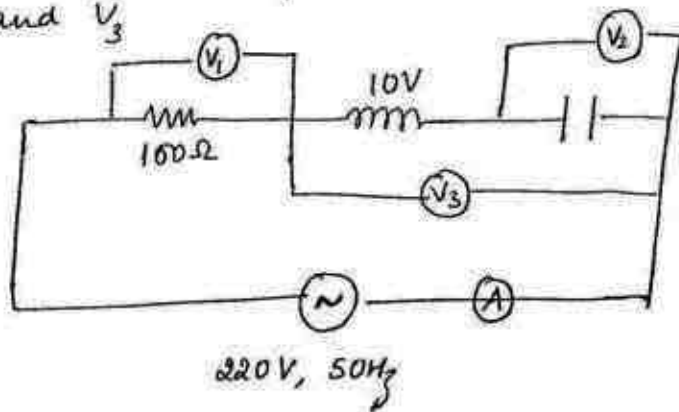c) if $\omega > \omega_r \rightarrow$ inductive

Q) In the given diagram, find readings of voltmeter V_1 , V_2 and V_3



Reading of ammeter is 2.2 A

$$V_1 = iR = 2.2 \times 100 = 220V = V_R$$

$$\therefore V_R = V \quad (\because \text{circuit is in resonance})$$

$$V_2 = V_C = V_L = 10V \quad (V_L = V_C \text{ in resonance})$$

$$V_3 = V_L - V_C = 10 - 10 = 0$$

Q) In series R-L-C circuit, resistance and capacitance are 10Ω and $1\mu F$ connected to an ac source 100V and $\frac{10}{\pi}$ Hz, then find voltage across inductor if circuit is in resonance / max current flows through the circuit / Impedance is min / power consumed is max / phase diff = 0

$$R = 10\Omega$$

$$C = 1\mu F$$

$$V = 100V$$

$$f = \frac{10}{\pi} \text{ Hz}$$

$$\therefore Z = \text{min (res.)}$$

$$\therefore V_L = V_C \quad (\text{i.e. resonance})$$

$$V_L = (V_C = i_n X_C) = \frac{V}{R} \times \frac{1}{2\pi f C}$$

$$= \frac{100}{10} \times \frac{1}{2\pi \times \frac{10}{\pi} \times 10^{-6}}$$

$$= 5 \times 10^5 \text{ V}$$

Q) In L-C oscillating circuit, capacitance becomes 4 times and inductance becomes 2 times then find by what times natural frequency will \uparrow ↓

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\omega' = \frac{1}{\sqrt{4C \times 2L}} = \frac{\omega}{2\sqrt{2}}$$

$$= 0.35 \omega$$

$$\left\{ \begin{array}{l} \therefore \frac{1}{\sqrt{2}} = 0.7 \end{array} \right\}$$


$\therefore \omega$ ↓ by $(1 - 0.35)\omega = 0.65\omega$

Half Power Point

These are the points in resonance curve where power consumed in circuit is half of the max power consumed at the time of resonance.

$$P = \frac{P_{\max}}{2} \quad \text{i.e.} \quad i^2 R = \frac{i_{\max}^2 R}{2} \quad [\because P = I^2 R]$$

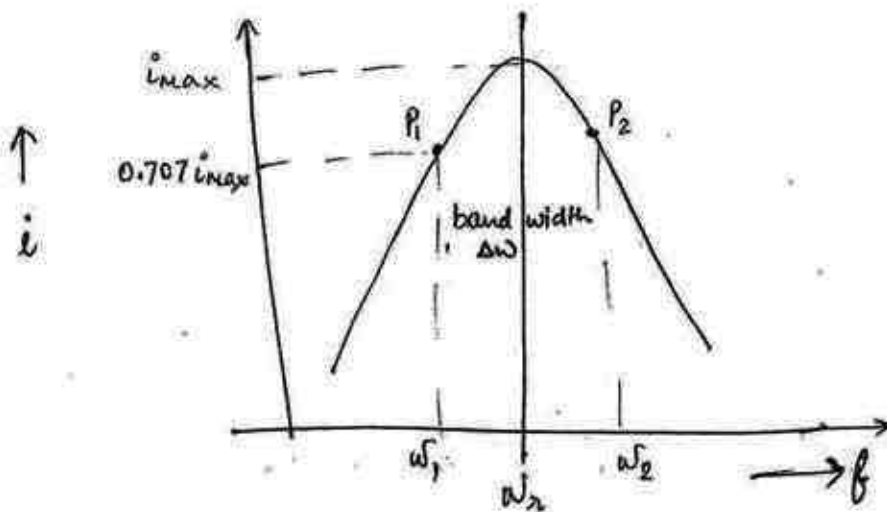
$$i = \frac{i_{\max}}{\sqrt{2}} = 0.707 i_{\max}$$



Resonance Half Power points (HPP)

; $\omega_1, \omega_2 =$ HPP frequency

Sharpness of resonance curve:

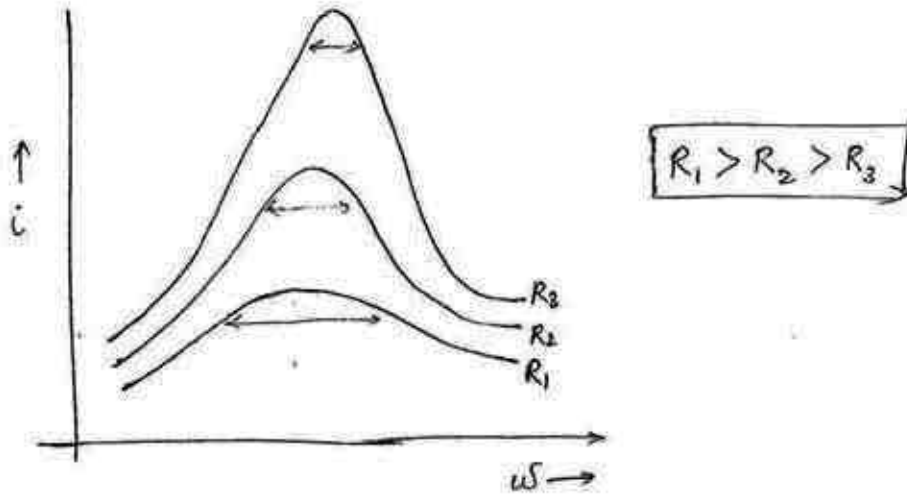

Quality factor:

It represents the quality/selectivity of an electrical signal and given by the ratio of resonating frequency to band width.

$$Q = \frac{\omega_r}{\Delta\omega}$$

$$Q = \frac{\omega_r L}{R} \quad (\because \Delta\omega L = R)$$

$$\therefore Q = \frac{X_L}{R} = \frac{X_C}{R} \quad \begin{array}{l} \because \text{its in} \\ \text{resonance} \\ \therefore X_L = X_C \end{array}$$

$$Q = \frac{1}{\sqrt{LC}} \times \frac{L}{R}$$

$$\Rightarrow Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\therefore R \downarrow \quad i_{\max} \uparrow \quad \underset{\text{(band width)}}{BW} \downarrow \quad \text{sharpness} \uparrow \quad \text{selectivity} \uparrow \quad Q \uparrow$$

Power in ac circuit

let instantaneous voltage and current are given by

$$V = V_0 \sin \omega t \quad i = i_0 \sin (\omega t \pm \phi)$$

the instantaneous power is given by

$$P = vi = V_0 \sin \omega t [i_0 \sin (\omega t \pm \phi)]$$

$$\begin{aligned} \therefore P &= V_0 I_0 \sin \omega t [\sin \omega t \cos \phi \pm \cos \omega t \sin \phi] \\ &= V_0 I_0 [\sin^2 \omega t \cos \phi \pm \cos \omega t \sin \omega t \sin \phi] \end{aligned}$$

So, average power consumed in circuit

$$\begin{aligned} \bar{P} &= \overline{V_0 I_0} [\overline{\sin^2 \omega t \cos \phi} \pm \overline{\cos \omega t \sin \omega t \sin \phi}] \\ &= V_0 I_0 \left[\frac{1}{2} \cos \phi \pm 0 \right] \end{aligned}$$

$$\therefore \boxed{\bar{P} = \frac{V_0 i_0 \cos \phi}{2}}$$

$$\bar{P} = \frac{V_0}{\sqrt{2}} \frac{i_0}{\sqrt{2}} \cos \phi$$

$$\bar{P} = V_{rms} i_{rms} \cos \phi$$

$$\therefore = (i_{rms})^2 \left(\frac{R}{Z} \right)$$

$$\therefore \boxed{\bar{P} = i_{rms}^2 R}$$

$$\therefore \bar{P} = \left(\frac{V_{rms}}{Z} \right)^2 R$$

$$\therefore \boxed{\bar{P} = \frac{V_{rms}^2 R}{R^2 + X^2}}$$

$$\therefore (X = X_L - X_C)$$

Power factor (PF)

In expression of avg. power, the multiplying factor $\cos \phi$ is called power factor


$$\boxed{P.f = \cos \phi = \frac{\bar{P}}{P_{rms}} = \left(\frac{R}{Z} \right) = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}}$$

$$0 \leq P.F. \leq 1$$

Power consumption in diff element:

- i) only R $\therefore \phi = 0 \therefore P.F = \cos \phi = 1 = \text{MAX}$
- ii) series R-L-C resonance $\phi = 0 \therefore P.F = \cos \phi = 1 = \text{MAX}$
- iii) if only L or C or LC both
 $\therefore \phi = \pm \pi/2 \therefore P.F = 0$


Wattless and working current

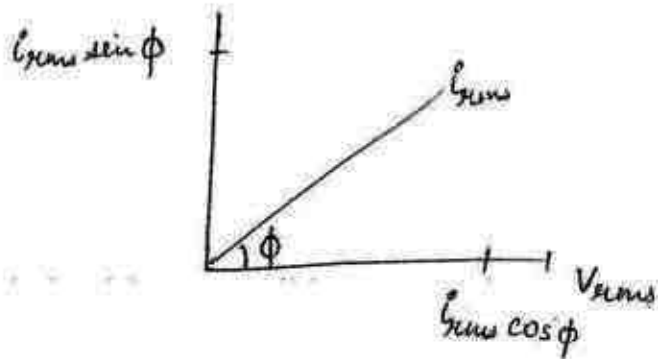

The component $i_{rms} \sin \phi$ which is having a phase diff of $\frac{\pi}{2}$ with the voltage consumes no power in circuit called wattless current

- a) $i_{rms} \sin \phi =$ wattless current
- b) $i_{rms} \cos \phi =$ working current

Choke coil

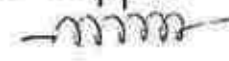- > It consist of a copper wire which is bend to form a helix 
- > Its working is based on wattless current
- > It is used to control / \downarrow the current in circuit

A practical choke coil will have very small resistance and high inductance





Resistance of ideal choke coil is assumed to be zero also called pure inductor.

choke coil are of 2 types:

air cored

Iron cored

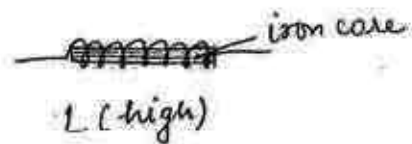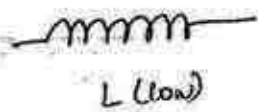

AC/DC instruments

AC instruments are based on heating effects of current cz heat released is independent of dirⁿ of current.

These instruments are also called hot wire instruments

DC instruments can't be used in AC circuit but AC instruments can be used in DC circuit

In DC instruments, scale is linear ($\theta \propto i$) but in AC instrument, scale is non-linear ~~($\theta \propto i$)~~.

($i \uparrow, H \uparrow, i^2 R t \uparrow, T \uparrow, l \uparrow \therefore \theta \uparrow$) $\therefore \theta \propto i^2$

Q) In series R-L-C circuit, resistance, inductive reactance and capacitive reactance are 2Ω , 6Ω , 4Ω respectively connected to an ac.

$$i = 2\sqrt{2} \sin(314t) \text{ A then find}$$

- i) reactance of circuit.
- ii) Phase diffⁿ b/w voltage & current
- iii) Power factor
- iv) Power consumed

$$i) X = X_L - X_C = 6 - 4 = 2\Omega$$

$$ii) \tan \phi = \frac{X_L - X_C}{R} = \frac{6 - 4}{2} = 1 \quad \therefore \phi = 45^\circ = \frac{\pi}{4}$$

$$iii) P.F = \cos \phi = \frac{1}{\sqrt{2}}$$


$$iv) P = i^2 R = 2^2 \times 2 = 8W$$

Q) In AC circuit, voltage and current are given by $V = V_0 \sin \omega t$ and $I = I_0 \cos \omega t$ then find Power consumed in the circuit.

$$\therefore \phi = \pi/2 \quad \therefore P = 0$$

$$\therefore \cos \frac{\pi}{2} = \cos 90^\circ = 0$$

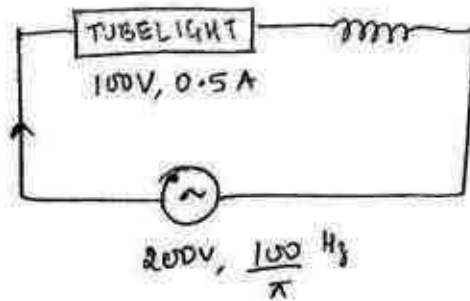Q) A tubelight operates at 100V, 0.5A connected to an AC source of 200V, $\frac{100}{\pi}$ Hz, then find inductance required to be connected in series with tubelight.



$$\therefore i = \frac{V}{\sqrt{R^2 + \omega^2 L^2}}$$

$$0.5 = \frac{200}{\sqrt{200^2 + \left(2\pi \frac{100}{\pi} L\right)^2}} \quad \therefore L = \sqrt{3} \text{ H}$$

Q) In AC circuit, voltage and current are $\overline{200 \text{ V}}, 2 \text{ A}$ and power consumption is $\overline{300 \text{ watt}}$. Then find Power factor of the circuit $\overline{\text{avg}}$

$$P.F = \frac{\overline{P}}{P_{\text{rms}}} = \frac{300}{200 \times 2} = \frac{3}{4} = 0.75$$