

# Current Electricity

## Article-1 DRIFT VELOCITY OF FLOW ELECTR.

A) Conductor without battery

> Free e-s in the metals are responsible for current conduction.


> Free e-s are set in random motion due to thermal effect of surrounding.

> Order of free e- density ~~is~~ in a metal is  $10^{28}$  electrons /  $m^3$  (independent of temp.)

This density is almost independent of temp.

> Mean free path in an metal is of the order of  $10 \text{ \AA}$  or  $10 \times 10^{-10} \text{ m} = 10^{-9} \text{ m}$  (distance b/w 2 collision)

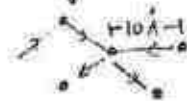( $\lambda$  depends upon nature of material)



> Thermal speed of electrons ( $V_T$ ):

$$\frac{3}{2} k_B T = \frac{1}{2} m_e V_T^2$$

$$k_B = 1.38 \times 10^{-23} \text{ J/K}$$

$$T = 300 \text{ K}, m_e = 9.1 \times 10^{-31} \text{ Kg}$$

$$\text{then } V_T \Rightarrow 10^5 \text{ m/s}$$

> Relaxation time ( $\tau$ ): It is average time taken

b/w 2 successive collision.

$$\text{(time) } \tau = \frac{\lambda}{v_f} = \frac{10^{-9} \text{ m}}{10^5 \text{ m/s}} = 10^{-14} \text{ sec}$$

> If battery is not connected then average velocity of free  $e^-$  group is 0.

$$\langle \vec{v} \rangle = \frac{\vec{v}_1 + \vec{v}_2 + \vec{v}_3 + \dots + \vec{v}_N}{N}$$

$$= \frac{\sum_{i=1}^N \vec{v}_i}{N} = \vec{0}$$


so that current in the wire is zero.

B) Conductor across battery

> When battery is connected, a uniform electric field is set inside the conductor which is responsible for drift in  $e^-$  group

> A current carrying wire remains electrically neutral so  $\vec{E}$  electric field outside the conductor is (it is opp. condition of electrostatics) zero
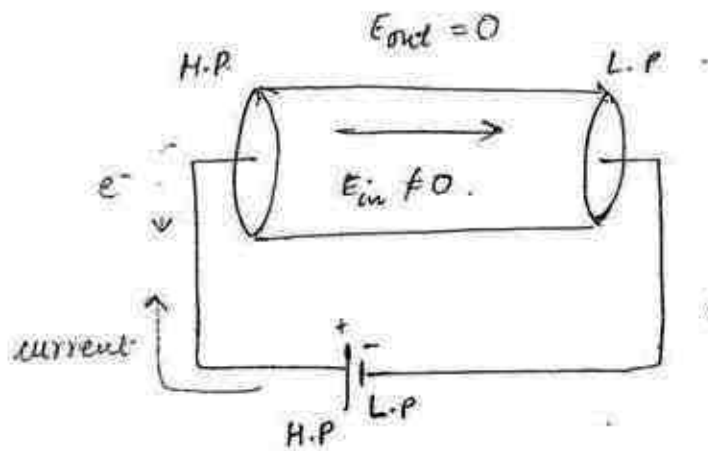
> Path of free  $e^-$ s b/w 2 collisions is usually curved path when  $\nabla$  battery is connected!



∴ flow of current is opposite to the flow of  $e^-$  (-ve charge)

Q) Derive expression of drift velocity of free  $e^-$ s in a metal

When battery is connected across a metallic wire, then a uniform electric field is created in the wire so all free  $e^-$ s experiences equal and constant acceleration

$$\vec{a} = \frac{q\vec{E}}{m} = \frac{-e\vec{E}}{m_e}$$

so, we can use equation of motion.

Consider an  $i^{\text{th}}$   $e^-$  just after its last collision. It's initial velocity is  $\vec{u}_i$  and after time interval  $t_i$ , velocity becomes  $\vec{v}_i$ , here  $\vec{v}_i = \vec{u}_i + \vec{a}t$

\* Drift velocity is the average velocity of group of free  $e^-$ s it means  $\vec{v}_{\text{drift}} = \langle \vec{v}_i \rangle = \langle \vec{u}_i \rangle + \vec{a} \langle t_i \rangle$

$\langle \vec{\mu}_i \rangle = \vec{0}$  because it has random values

$\langle t_i \rangle = \tau$  (Relaxation time)

$$\text{so, } \vec{V}_{\text{drift}} = \vec{a}\tau = \left( \frac{-e\vec{E}}{m_e} \right) \tau$$

$$\boxed{|\vec{V}_d| = \frac{e\tau}{m_e} E} \quad (v = at) \quad \text{its magnitude } \because I \text{ is scalar}$$

conclusion:

The magnitude of drift velocity is independent of time  $\tau = \text{constant} = 10^{-14} \text{ sec}$  and order of drift velocity is

$10^{-2} \frac{\text{m}}{\text{s}}$  or  $10^{-3} \text{ m/s}$  but electric field

in the wire propagates with the speed of light. so, it takes very negligible time in switching (ON and OFF)

$$\star \boxed{V_d = \mu E} \quad \mu = \frac{e\tau}{m_e} = \text{mobility constant}$$

$\mu$  depends upon nature and temperature of material ~~and~~ wire

Article : 2

$$I = n e A V_d$$

no of e<sup>-</sup> per unit vol

> Rate of flow of charge is called electric current

$$I = \frac{dq}{dt}$$

$$I = \frac{\Delta q}{\Delta t} = \frac{q}{t} \quad \text{when } I = \text{constant}$$

$$* \quad q = \int_{t_1}^{t_2} I dt$$

Q) current in a wire is  $I = (2t - 3t^2) A$

How much charge will pass through a cross section b/w  $t = 2s$  to  $t = 3s$

$$\therefore I = \frac{dq}{dt}$$

$$\therefore q = \int_{t_1}^{t_2} I dt = \int_2^3 (2t - 3t^2) dt$$

$$= \left[ \frac{2t^2}{2} - \frac{3t^3}{3} \right]_2^3 \Rightarrow \left[ t^2 - t^3 \right]_2^3$$

$$(3^2 - 3^3) - (2^2 - 2^3) \Rightarrow (9 - 27) - (4 - 8)$$

$$(-18) - (-4) \Rightarrow -18 + 4 = \boxed{-14 C}$$

Q1) An  $e^-$  is moving in a circular orbit of radius  $R$ . Its frequency of rotation is  $\nu$ . Calculate magnitude of current associated with the  $e^-$ .



$$T \longrightarrow e$$

$$I \longrightarrow \frac{e}{T} = I$$

$$\therefore \boxed{I = e\nu}$$

$$\boxed{T = \frac{2\pi R}{\nu}}$$


$$\therefore I = \frac{e}{T} = \frac{e}{\left(\frac{2\pi R}{\nu}\right)} = \boxed{\frac{e\nu}{2\pi R} = I}$$

- \* In metals only free  $e^-$ s are responsible for current conduction.
- \* In electrolytes +ve and -ve ions are responsible for current conduction eg  $\text{NaCl} \rightarrow \text{Na}^+ + \text{Cl}^- (\text{aq})$
- \* In gases +ve ions and  $e^-$ s are responsible for current conduction  
eg  $\text{H} \rightarrow \text{H}^+ + e^-$

$\Rightarrow$  Electric current is scalar

In case of liquid / gases:


Case I

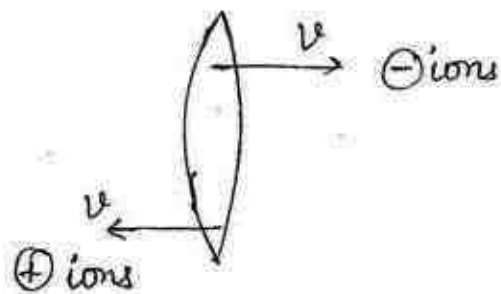

$$I_{net} = I_1 + I_2 (\leftarrow)$$

current moves in the dir<sup>n</sup> of the +ve and in the oppo. dir<sup>n</sup> of -ve

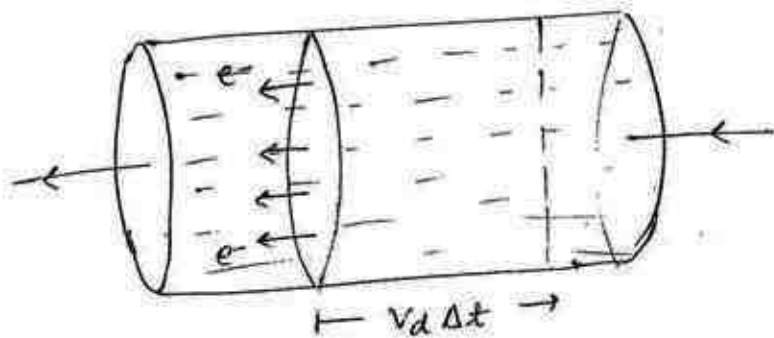Q) In a conducting wire, area of cross section is  $A$  and free  $e^-$  density is  $n$ . and drift velocity is  $v_d$ . Find expression of electric current in the wire.



group of  $e^-$ s moves with constant velocity and it travels  $v_d \Delta t$  distance in time interval  $\Delta t$ . so charge enclosed in the vol<sup>m</sup>,  $A(v_d \Delta t)$  will pass through the cross sectional area and value of charge is

$$\Delta q = A(v_d \Delta t) \times n \times e$$

$$\therefore \frac{\Delta q}{\Delta t} = I = neA \cdot v_d$$

Current density ( $\vec{J}$ ):

It is current passing through per unit area of cross section.

It's unit is  $A/m^2$  and it is a vector quantity. Its direction is in the direction of electric field.

$$I = neA v_d$$

$$\therefore J = \frac{I}{A} = \frac{neA v_d}{A} = \boxed{ne v_d}$$

$$J = ne (\mu E)$$

$$J = ne \left[ \frac{e\tau}{m_e} \right] E = \left( \frac{ne^2\tau}{m_e} \right) E$$

$$J = \sigma E$$

$$\therefore \boxed{\vec{J} = \sigma \vec{E}}$$

here  $\sigma = \frac{ne^2\tau}{m_e}$   
 ↓  
 conductivity.

$$\rho = \frac{1}{\sigma} = \frac{m_e}{ne^2\tau}$$

resistivity

is in specific resistance.



conclusion:

>  $\sigma$  and  $\rho$  depends upon nature and temp. of material


> \* In case of metals, if temperature  $\uparrow$ es, then relaxation time  $\downarrow$ es so  $\sigma \downarrow$ es and  $\rho \uparrow$ es.

> \* In insulators and semi-conductor, if temp  $\uparrow$ es, then  $n \uparrow$ es,  $\sigma \uparrow$ es and  $\rho \downarrow$ es.

>  $I = \oint \vec{J} \cdot d\vec{A}$

It means current is flux of current density

Q1)

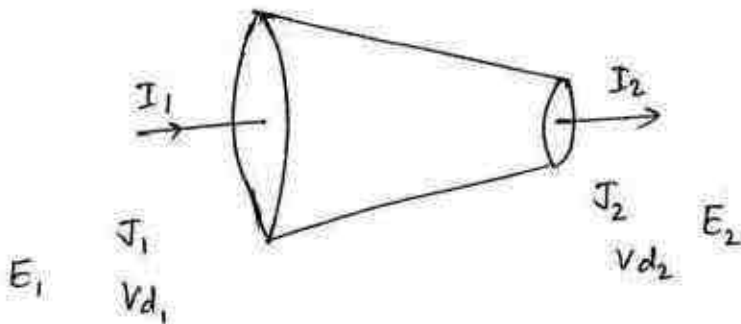

i)  $I_1 = I_2$  (incoming <sup>current</sup> charge = outgoing charge)

ii)  $J_1 < J_2$  ( $J \propto \frac{1}{A}$ )

iii)  $E_1 < E_2$  ( ~~$V_d \propto \frac{1}{A}$~~ ) [ $E \propto J$ ]

iv)  $V_{d1} < V_{d2}$  ( $E \propto V_d$ ) [ $V_d \propto E$ ]


Article 3

Ohm's law

\* we talk of potential as a reference

∴ V as potential, makes no sense.

It's potential difference

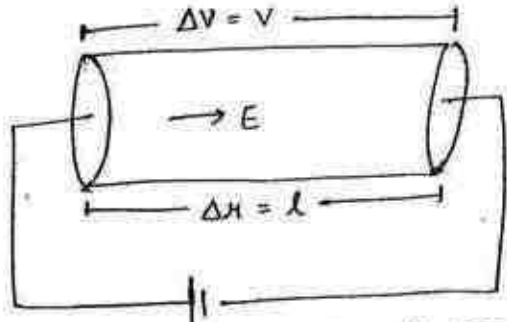

$$J = \sigma E$$

$$\frac{I}{A} = \frac{1}{\rho} \left( \frac{\Delta V}{\Delta x} \right)$$


$$\frac{I}{A} = \frac{1}{\rho} \times \frac{V}{l}$$

$$\therefore V = \frac{\rho l}{A} I$$

$$\boxed{V = IR} \quad \therefore R = \frac{\rho l}{A}$$

If R = constant

V ∝ I (Ohm's law)

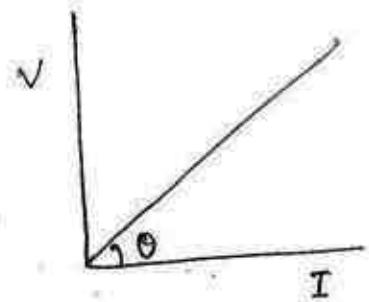

$$\text{slope} = \tan \theta = \frac{V}{I} = R$$

Conclusion :

- i) Ohm's law is not a fundamental law.
- ii) Semiconductor device doesn't follow Ohm's law
- iii) Resistance depends upon ⇒ nature, Temp, length and area of cross section of wire but

∴ dependent of l and A

Q) Resistance of a wire is  $R$ . If it is stretched then its length becomes  $n$  times of initial, find its final resistance

$$\therefore R = \frac{\rho l}{A}$$

$$\therefore R = \frac{\rho l'}{A'} = \frac{\rho n l}{A/n}$$

$$= n^2 \frac{\rho l}{A} = \boxed{n^2 R}$$

$$\left[ \begin{array}{l} \therefore V_1 = V_2 \\ \therefore A \times l = n l \times A' \\ \therefore A' = \frac{A \times l}{n l} = \frac{A}{n} \end{array} \right.$$

Q) When a wire of resistance  $R$  is stretched its radius of cross section becomes  $\frac{1}{n}$  times of initial. Find its final resistance

$$\therefore V_1 = V_2$$

$$\therefore A \times l = A' l'$$

$$l' = \frac{\pi r^2 l}{\pi \left(\frac{r}{n}\right)^2}$$

$$\therefore l' = n^2 l$$

$$\therefore R = \frac{\rho l'}{A'} = \frac{\rho n^2 l}{\pi \left(\frac{r}{n}\right)^2}$$

$$= \frac{n^4 \rho l}{\pi r^2} = n^4 \frac{\rho l}{A}$$

$$= \boxed{n^4 R}$$

Q) When a wire is stretched, its length increases by 50%. Find % change in its resistance.

$$l' = \frac{l \times 50}{100} = \frac{l}{2} \Rightarrow l + \frac{l}{2} = \frac{3l}{2}$$

$$\therefore V_1 = V_2$$

$$A \times l = A' \times l'$$

$$\therefore A' = \frac{A \times l \times 2}{3l} = \frac{2A}{3}$$

$$\therefore R = \frac{\rho l'}{A'} = \frac{\rho \frac{3l}{2}}{\frac{2A}{3}} = \frac{9}{4} \frac{\rho l}{A} = \frac{9}{4} R$$

$$\therefore \% \text{ change} = \frac{\Delta R}{R} \times 100$$

$$= \frac{\frac{9}{4} R - R}{R} \times 100$$

$$= \frac{5R}{4R} \times 100 = 25 \times 5 = \boxed{125\%}$$

$$* \boxed{\text{Change} \Rightarrow \Delta R} \Rightarrow R_f - R_i$$

$$* \boxed{\text{Fractional change} \Rightarrow \frac{\Delta R}{R}} = \frac{R_f - R_i}{R_i}$$

$$* \boxed{\% \text{ change} \Rightarrow \frac{\Delta R}{R} \times 100} \Rightarrow \frac{R_f - R_i}{R_i} \times 100$$

Q) There are 3 copper wire, ratio of their length is 1:2:3 and ratio of their mass is ~~3:2:1~~ 3:1:2. Find ratio of resistance

$$R = \frac{\rho l}{A}$$

$$\therefore R = \frac{\rho l^2}{(\text{Vol}^M)} \quad \left[ \because \text{Vol}^M = A \times l \quad \therefore A = \frac{\text{Vol}^M}{l} \right]$$

$$R = \frac{\rho l^2}{\left(\frac{m}{d}\right)} \Rightarrow \frac{\rho l^2 d}{m}, \quad d = \text{density.}$$

$$\therefore R \propto \frac{l^2}{m} \quad \therefore R_1 : R_2 : R_3 = \frac{1^2}{3} : \frac{2^2}{1} : \frac{3^2}{2}$$

$$\frac{1}{3} : \frac{4}{1} : \frac{9}{2} \Rightarrow \boxed{2 : 24 : 27}$$

Q) There are three copper wire. Ratio of their area of cross section is 1:1:2 and ratio of their mass is 1:2:3


$$\therefore R = \frac{\rho l}{A} \Rightarrow \frac{\rho (\text{Vol}^M)}{A A} = \frac{\rho \text{Vol}^M}{A^2} \quad \left[ \because l = \frac{\text{Vol}^M}{A} \right]$$

$$\therefore R = \frac{\rho \left(\frac{m}{d}\right)}{A^2} \quad \left[ \because \text{Vol}^M = \frac{m}{d} \right]$$

$$\therefore R \propto \frac{m}{A^2} \Rightarrow \frac{1}{1^2} : \frac{2}{1^2} : \frac{3}{2^2} \Rightarrow 1 : 2 : \frac{3}{4}$$

$$\therefore R_1 : R_2 : R_3 \Rightarrow \boxed{4 : 8 : 3}$$
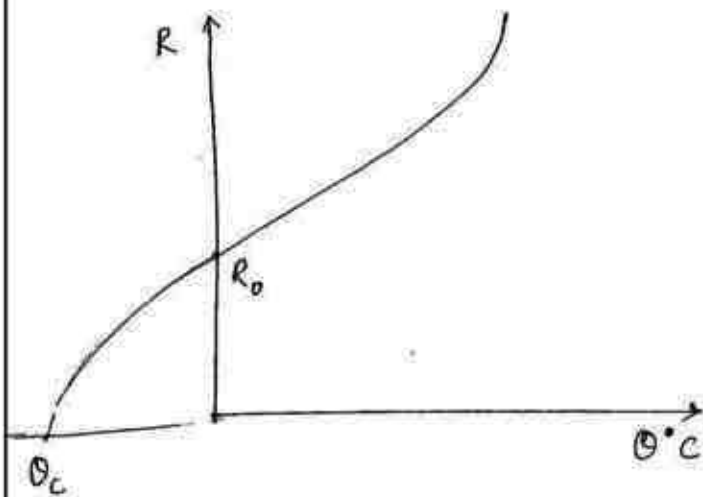
## Variation in resistance with temperature



$$R_{t_2} = R_{t_1} [1 + \alpha(t_2 - t_1)]$$

$$R_{t_2} = R_{t_1} + R_{t_1} \alpha (t_2 - t_1)$$

$$\therefore \frac{R_{t_2} - R_{t_1}}{R_{t_1} (t_2 - t_1)} = \alpha$$

### Conclusion:

i) graph is not a perfect straight line but in numerical it can be taken as approx a straight line

ii)  $\alpha$  is called, temperature coefficient of resistance. It is defined as fractional change in resistance for unit change in temperature. Its unit is  $\text{per}^\circ\text{C}$  or  $\text{per K}$  ( $\because$  change is same) i.e.  $\alpha = \frac{\Delta R}{R(t)}$

iii)  $\theta_c$  is critical temp, at this temp, resistance becomes zero and conductor becomes super conductor

$$T_0 = 4.2 \text{ K}$$

Q) Temp coefficient of a wire is  $0.00125$  per  $^{\circ}\text{C}$ .  
 Its resistance at  $300\text{ K}$  is  $1\ \Omega$ . Find at  
 which temp its resistance will be  $2\ \Omega$

$$\therefore R_{t_2} = R_{t_1} [1 + \alpha (t_2 - t_1)]$$

$$2 = 1 [1 + \alpha (t_2 - t_1)]$$

$$1 = \alpha (t_2 - t_1)$$


$$t_2 - t_1 = \frac{1}{\alpha} = 800$$

$$t_2 = 800 + t_1$$

$$= 800 + 300 = \boxed{1100}$$

Q) There are 2 wires of Temp coefficient ( $\alpha$ )  
 $\ast$  and ( $-\beta$ ). If effective resistance of their  
 series combination is independent of temp.  
 then find ratio of their resistances at  $0^{\circ}\text{C}$

let the system be at  $t$  temp

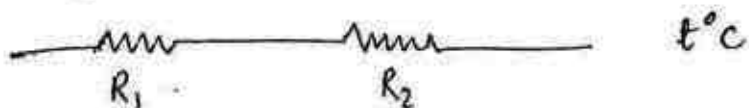

$$R_{\text{net}} = R_1 + R_2$$

$$= R_{01} [1 + \alpha (t - 0)] + R_{02} [1 + (-\beta) (t - 0)]$$

$$= (R_{01} + R_{02}) + t [\alpha R_{01} - \beta R_{02}]$$

If  $R_{net}$  is independent of temp then

$$R_{01} \alpha - R_{02} \beta = 0$$

$$\therefore \frac{R_{01}}{R_{02}} = \frac{\beta}{\alpha}$$

Q) There are 2 wires with temp. coefficient  $\alpha_1$  and  $\alpha_2$  their resistance at  $0^\circ\text{C}$  are  $R_{01}$  and  $R_{02}$ . Find equivalent temp. coefficient of their series combination.

$$R_{eq} = R_1 + R_2 \quad (\because \text{series})$$

$$= R_{01} [1 + \alpha_1(t-0)] + R_{02} [1 + \alpha_2(t-0)]$$


$$= (R_{01} + R_{02}) + t(R_{01}\alpha_1 + R_{02}\alpha_2)$$

$$= (R_{01} + R_{02}) \left[ 1 + \frac{(R_{01}\alpha_1 + R_{02}\alpha_2)}{R_{01} + R_{02}} t \right]$$

$$\therefore \alpha_{eq} = \frac{R_{01}\alpha_1 + R_{02}\alpha_2}{R_{01} + R_{02}}$$



## (A) Series combination of Resistance

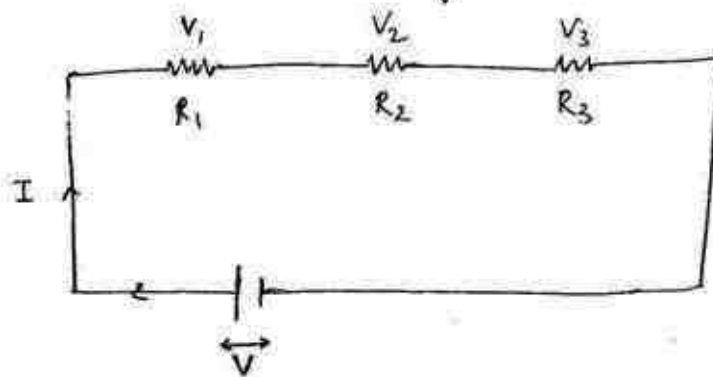

$$\therefore V = V_1 + V_2 + V_3$$

$$I R_{eq} = IR_1 + IR_2 + IR_3$$

$$R_{eq} = R_1 + R_2 + R_3$$

### Imp. Points

- i) If there is a single loop without any branch then all resistances are connected in series then current in the loop is


$$I = \frac{V_{net}}{R_{net}} = \frac{V_{eq}}{R_{eq}}$$

This is the current supplied by battery and current in each elements

- ii) If all series resistance are equal and no. of resistance are  $N$ , then  $R_{eq} = NR$

- iii) In series combination,  $R_{eq} >$  resistance of greatest value

(B) Parallel combination of resistances.

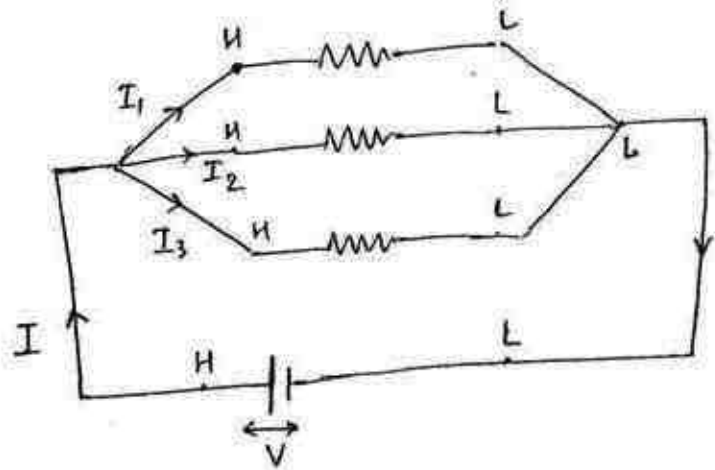

$$I = I_1 + I_2 + I_3$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Imp points:

i) Initial end of all resistances should be at common point as well as final end of all resistance should be at common point.

ii) Potential across each element are equal

iii) If there are  $N$  resistance, each of value  $R$ , then

$$R_{eq} = \frac{R}{N}$$


iv) If there are only 2 parallel wire





$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow \therefore R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \text{ is Product}$$

v) In parallel combination,

$R_{eq} < \text{smallest value}$

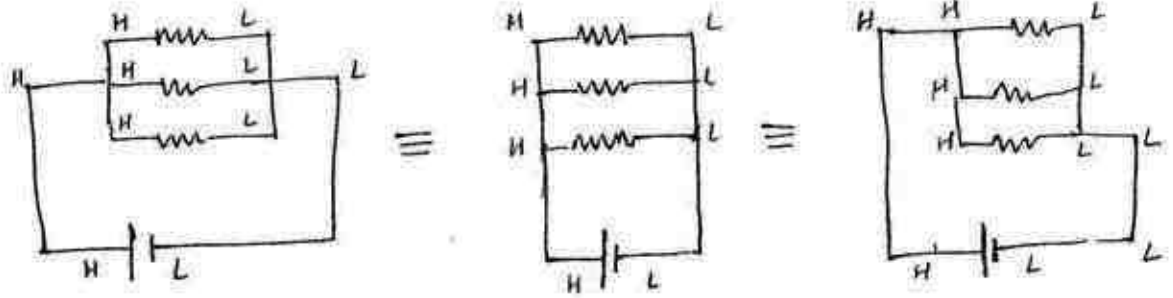

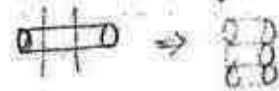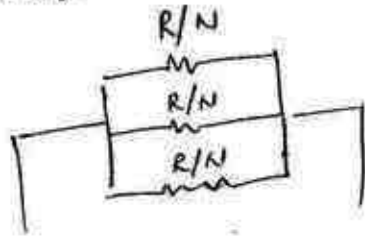Q) Resistance of a wire is  $R$ . It is cut into  $N$  equal parts of length. Now these parts are connected in parallel with each other. Find equivalent resistance of combination.



$$R = \frac{\rho l}{A}$$


$$R' = \frac{\rho(l)}{n(nA)} = \frac{\rho}{n^2}$$

$$R_{eq} = \frac{R'}{N} = \frac{R/N}{N} = \frac{R}{N^2}$$

Q) There are 2 wires of equal length and equal area of cross section. Their resistivity are  $\rho_1$  and  $\rho_2$  respectively. Find equivalent resistivity of their combination. if they are connected in

- series
- parallel

i)

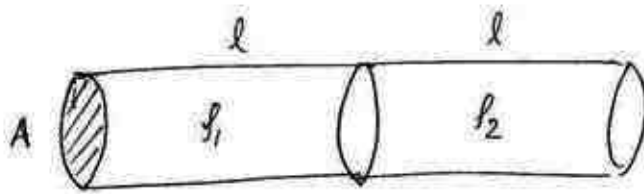


$$R_{eq} = R_1 + R_2$$

$$\frac{R_{eq} (2l)}{A} = \frac{R_1 l}{A} + \frac{R_2 l}{A}$$

$$\therefore R_{eq} = \frac{R_1 + R_2}{2} \quad (\text{A.M}) \text{ Arithmetic mean}$$

ii)

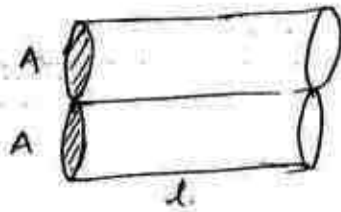

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\frac{R_{eq} l}{2A} = \frac{\left(\frac{R_1 l}{A}\right) \left(\frac{R_2 l}{A}\right)}{\frac{R_1 l}{A} + \frac{R_2 l}{A}}$$

$$\therefore R_{eq} = \frac{2 R_1 R_2}{R_1 + R_2} \quad (\text{H.M}) \text{ Harmonic mean}$$

Article : 4 (A) Kirchoff's law - current (KCL)

1) Kirchoff's first law (or current law or junction law)

At any junction of electric circuit, algebraic sum of all current must be zero.  
It is based on charge conservation.


$$\sum_{\text{junction}} I = 0$$

OR

$$|I_{in}| = |I_{out}|$$

$$I_1 + I_2 = I_3 + I_4$$

Q)

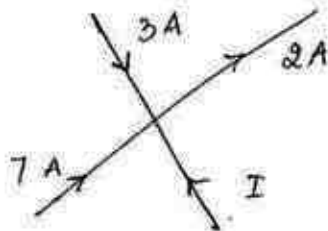


$$7 + 3 + I = 0$$

$$\therefore I = -10$$

here, -ve indicates that actual flow of current is opposite to given dir.


Q)

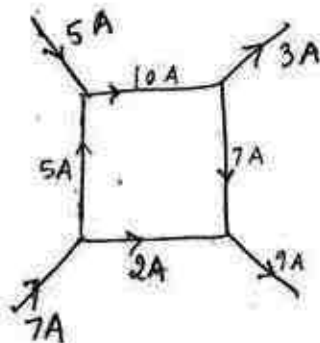

Incoming = Outcoming

$$5 + 7 = 3 + I$$

$$\therefore I = 9A$$

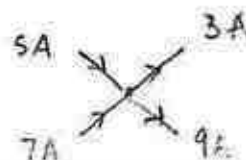


Ⓐ Kirchhoff's voltage law (KVL) /  
Kirchhoff's second law /  
Kirchhoff's loop law

\* Algebraic sum of all potential difference (including resistance and battery) in a loop must be zero.

It is based on energy conservation.

$$\sum_{\text{loop}} V = 0$$

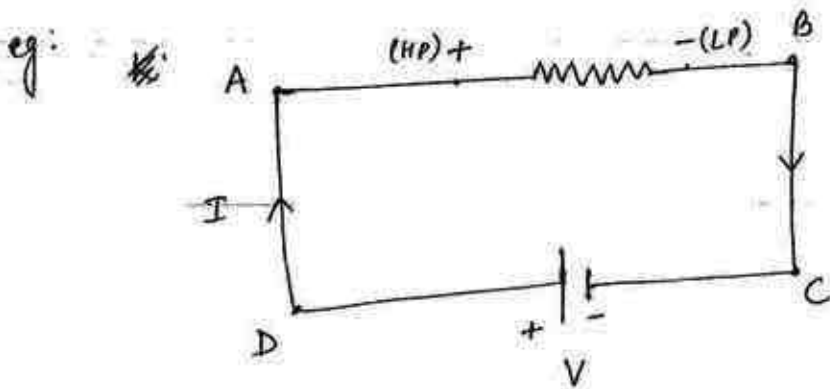

KVL in the loop ABCDA :

$$V_A - IR + V = V_A$$

$$\therefore -IR + V = 0$$

$$\text{so } \sum_{\text{loop}} V = 0$$

How to apply KVL :


- i) select direction of current
- ii) put  $\oplus$ ve and  $\ominus$ ve sign across each element
- iii)  $\oplus$ ve and  $\ominus$ ve sign on the resistance (resistor) depends upon dir<sup>n</sup> of current but  $\oplus$ ve and  $\ominus$ ve sign across battery is independent of dir<sup>n</sup> of current.



- iii) select a loop or part of loop to apply KVL and selection of loop is independent of dir<sup>n</sup> of current

iv) Apply KVL

Q)

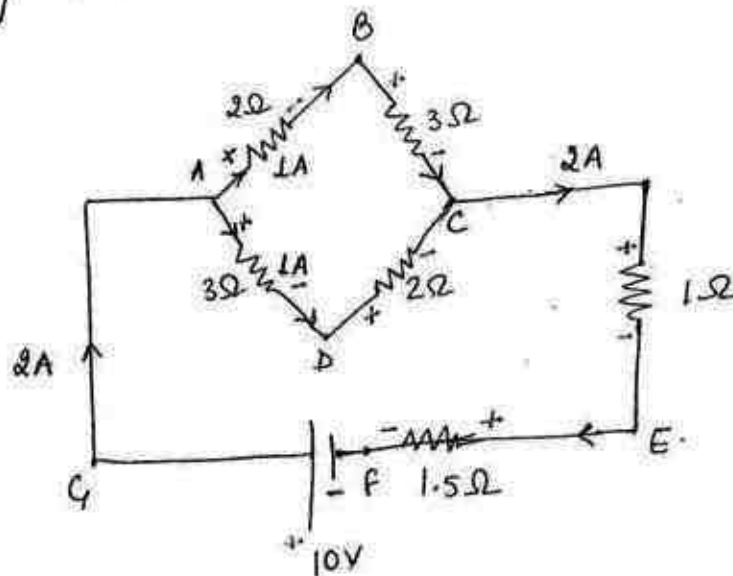

$$\therefore V = IR$$

$$\therefore I = \frac{V_{\text{net}}}{R_{\text{net}}} = \frac{10}{5} = 2A.$$

Find:

i)  $V_A - V_C$

KVL in ABC

$$V_A - 2 \times 1 - 3 \times 1 = V_C$$

$$\therefore V_A - V_C = 3 + 2 = \boxed{5V}$$

ii)  $V_B - V_D$

KVL in BCD

$$V_B - 3 + 2 = V_D$$

$$\therefore V_B - V_D = 3 - 2 = \boxed{1V}$$

iii)  $V_D - V_E$

KVL in DCE

$$V_D - 2 - 2 = V_E$$

$$\therefore V_D - V_E = \boxed{4V}$$

iv)  $V_A - V_F$

KVL in ABCEP

$$V_A - 2 - 3 - 2 - 3 = V_F$$


OR KVL in AGF

$$V_A - 10 = V_F$$

$$\therefore V_A - V_F = \boxed{10V}$$



Q)

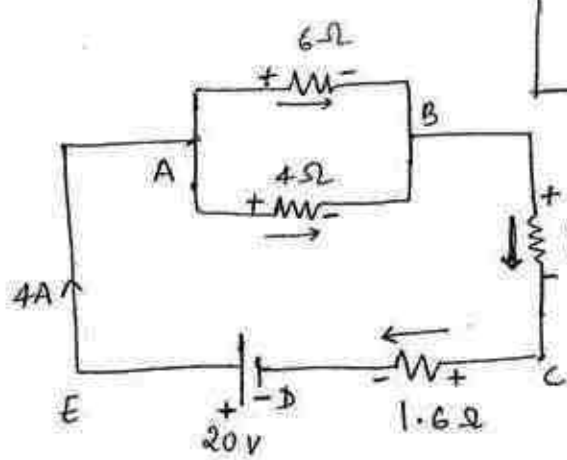

Current is in the  
inverse ratio of resistances

$$\therefore I \text{ across } 6\Omega = \frac{4 \times 4}{10} = 1.6$$

$$I \text{ across } 4\Omega = \frac{6}{10} \times 4 = 2.4$$

$$\therefore V = IR$$

$$\therefore I = \frac{V_{\text{net}}}{R_{\text{net}}} = \frac{20}{5} = 4A$$

i)  $V_A - V_B$

KVL in AB

$$V_A - IR = V_B$$

$$V_A - V_B = IR = 4 \times 2.4 = \boxed{9.6V}$$

ii)  $V_A - V_C$

KVL in ADC

$$V_A - 20V + 1.6 \times 4 = V_C$$

$$\therefore V_A - V_C = 20 - 6.4 = \boxed{13.6V}$$


iii)  $V_A - V_D$

KVL in AED

$$V_A - 20V = V_D$$

$$\therefore V_A - V_D = \boxed{20V}$$

Q1)

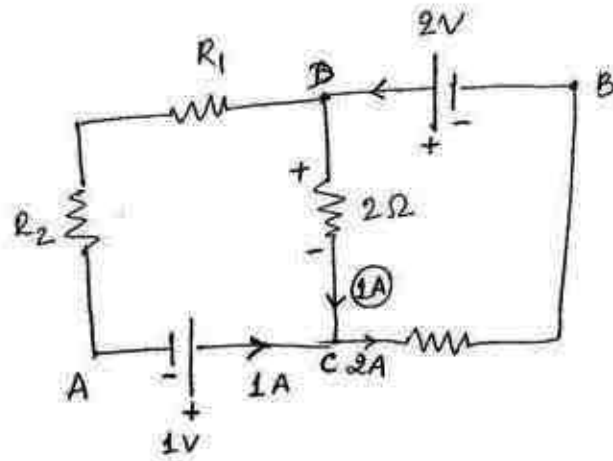

If  $V_A = 0$ . Find  $V_B$

KVL in ACBB


$$V_A + 1 + 2 - 2 = V_B$$

$$\therefore V_A - V_B = -1$$

$$0 - V_B = -1$$

$$\therefore V_B = 1$$

Q2)

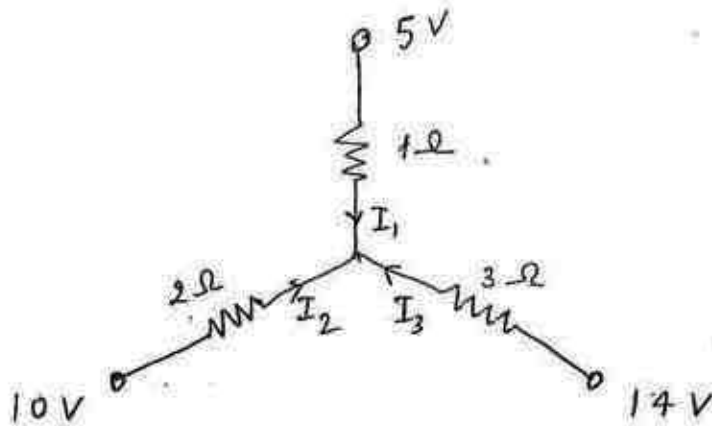

Find  $I_1$ ,  $I_2$  and  $I_3$ .

Find potential at junction

$$I_1 + I_2 + I_3 = 0 \quad (\text{KCL})$$

$$\left(\frac{5-x}{1}\right) + \left(\frac{10-x}{2}\right) + \left(\frac{14-x}{3}\right) = 0$$

$$\therefore \frac{6(5-x) + 3(10-x) + 2(14-x)}{6} = 0$$

$$\therefore 30 - 6x + 30 - 3x + 28 - 2x = 0$$

$$\therefore 88 - 11x = 0$$

$$\therefore 11(8 - x) = 0$$


$$\therefore x = 8$$

$$I_1 = \frac{5-8}{1} = -3A$$

$$I_2 = \frac{10-8}{2} = 1A$$

$$I_3 = \frac{14-8}{2} = \frac{6}{2} = 3A$$

\* Q))

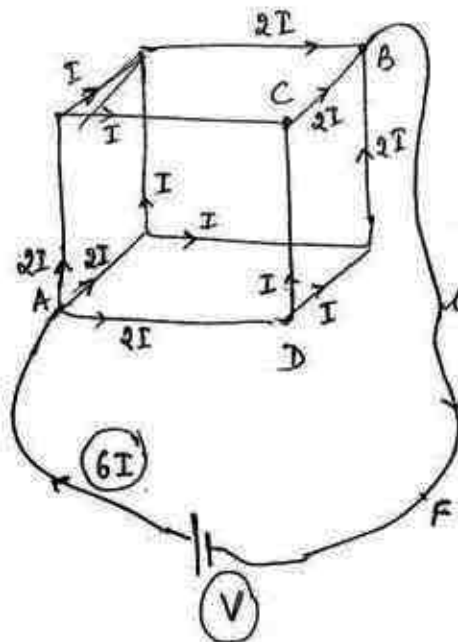

There are 12 identical wires each of resistance R in a cubical network

6I distribute the charges at point A and then at point B. and then manipulate the charges within

$$i) \quad \therefore R_{eq} = \frac{V}{6I} \quad \text{--- (1)}$$

KVL in loop ADCBFA

$$\cancel{V_A} - 2IR - IR - 2IR + V = \cancel{V_A}$$


$$\therefore V = 5IR$$

$$\therefore \frac{V}{I} = 5R$$

Putting in eq (1)

$$R_{eq} = \frac{1}{6} \left( \frac{V}{I} \right) = \frac{1}{6} 5R = \boxed{\frac{5R}{6}} \quad \star$$

ii)

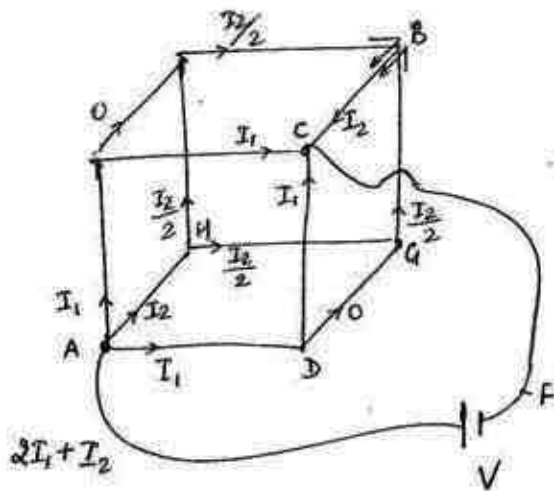

$$R_{eq} = \frac{V}{2I_1 + I_2} \quad \text{--- (1)}$$

Loop ADCFA

$$\cancel{V_A} - I_1 R - I_1 R + V = \cancel{V_A}$$

$$\therefore V = 2I_1 R \quad \therefore \frac{V}{I_1} = 2R \quad \text{--- (11)}$$

loop ADGHA

$$V_A - I_1 R + \left(\frac{I_2}{2}\right)R + I_2 R = V_A$$

$$\therefore I_1 R = \frac{I_2 R}{2} + I_2 R = R \frac{(I_2 + 2I_2)}{2} = \frac{3I_2 R}{2}$$


$$I_1 R = \frac{3I_2 R}{2}$$

$$\therefore I_2 = \frac{2}{3} I_1 \quad \text{put in eq (1)}$$

$$\therefore R_{eq} = \frac{V}{2I_1 + \left(\frac{2}{3}I_1\right)} = \frac{3}{8} \left(\frac{V}{I_1}\right) = \frac{3}{8} 2R$$

$$\therefore R_{eq} = \frac{3}{4} R$$

iii)

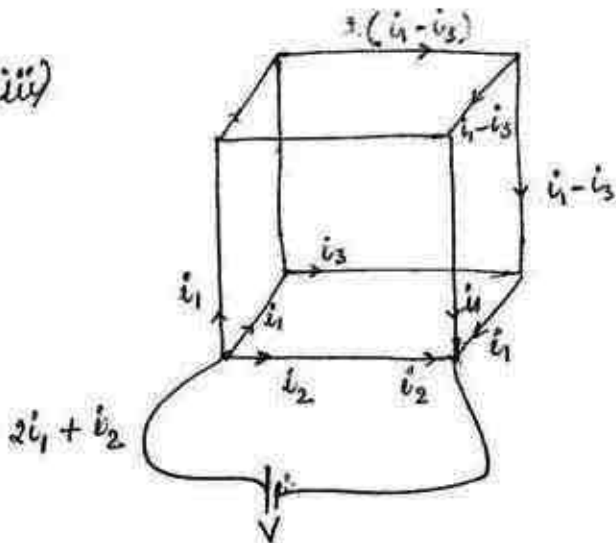

Conclusion


$$R > \frac{5}{6} R > \frac{3}{4} R > \frac{7}{12} R$$

$$R_{eq} = \frac{V}{2I_1 + I_2}$$

On solving, we get

$$\frac{7}{12} R$$

Q1) A part of network is given

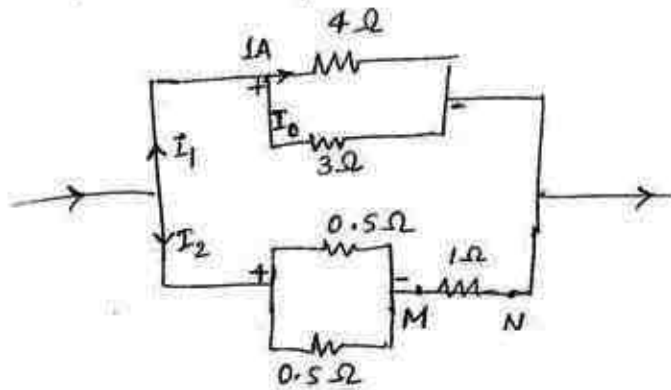

Calculate  
 $V_M - V_N$

$$1 \times 4 = I_0 (3) \quad \left[ \begin{array}{l} \because V_1 = V_2 \\ I_1 R_1 = I_2 R_2 \end{array} \right]$$

$$\therefore I_0 = \frac{4}{3}$$

$$\begin{aligned} I_1 &= 1A + I_0 \\ &= 1 + \frac{4}{3} = \frac{7A}{3} \end{aligned}$$

$$\therefore I_1 \times R_1 = I_2 \times R_2 \quad (\because \text{they are in parallel})$$

$$\begin{aligned} \frac{7}{3} \times \frac{12}{7} &= I_2 \times \frac{5}{4} \\ \therefore I_2 &= \frac{7}{3} \times \frac{12}{7} \times \frac{4}{5} = \frac{16}{5} \end{aligned} \quad \left[ \begin{array}{l} R_1 = \frac{4 \times 3}{4+3} = \frac{12}{7} \Omega \\ R_2 = \frac{0.5 \times 0.5}{0.5+0.5} + 1 \\ = 0.25 + 1 = 1.25 = \frac{5}{4} \end{array} \right]$$

By KVL

$$V_M + \frac{16}{5} \times \frac{1}{4} - \frac{7}{3} \times \frac{12}{7} = V_N$$

$$\therefore V_M - V_N = \frac{12}{3} - \frac{4}{5} = \frac{60-12}{15} = \frac{48}{15} = \boxed{\frac{16}{5}}$$


# Article : 5 Cell and Battery

i) Ideal cell:




EMF : Electro motive force (in volt)  $\neq$  force  
Internal resistance ( $r$ ) = 0

ii) Real cell:

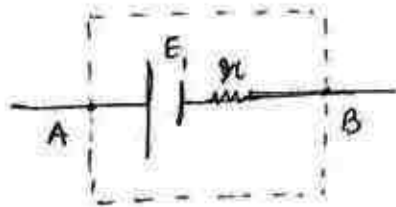

$V_A - V_B = \text{TPD}$  (Terminal Potential diff)  
always  $\oplus$ ve value

\* iii) Discharging of a cell:

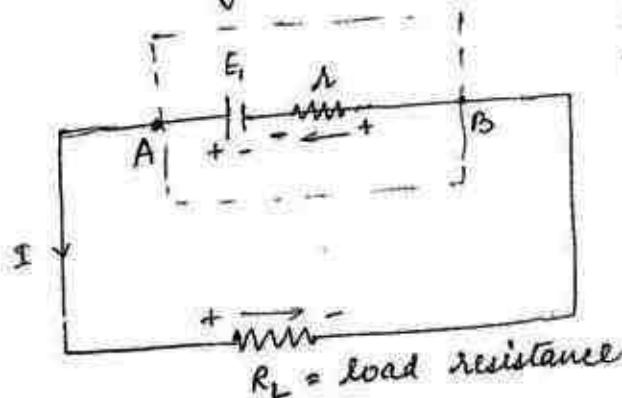

current flows out from  
the +ve terminal of the  
battery (Discharging)

KVL A to B (via battery)

$$V_A - E_1 + I r = V_B$$

$$\therefore V_A - V_B = E_1 - I r$$

$$\therefore \text{TPD} = E_1 - I r$$

KVL A to B (via  $R_L$ )

$$V_A - IR_L = V_B$$

$$[V_A - V_B = IR_L]$$

Current feeds all the resistance whereas TPD feeds only the load resistance


\*\*\*  
∴

$$I = \frac{E_1}{\lambda + R_L} = \frac{TPD}{R_L}$$

NEET 2013

> If cell is not ~~is~~ in used ( $I=0$ ), then its TPD is its EMF

(v) charging of a cell

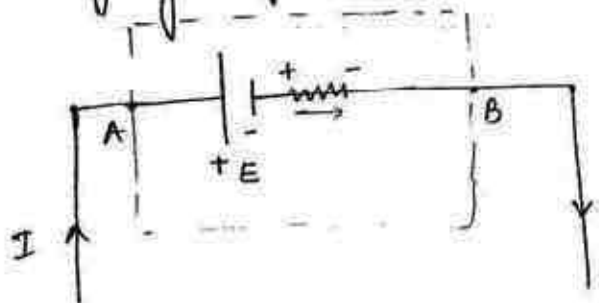

Current enters into the +ve terminal of the battery

KVL A to B

$$V_A - E - I r = V_B$$

$$\therefore V_A - V_B = I r + E$$

$$\therefore \boxed{TPD = E + I r}$$

Here,  $TPD > E$



Points to remember

TPD may be greater than or less than EMF of the cell

charging  $\Rightarrow$  greater

discharging  $\Rightarrow$  lesser

Q) EMF of a cell is 10V. It is connected across a load of resistance  $2\Omega$  if current supplied by battery is 4A, then find internal resistance of the cell.

$$I = \frac{E}{r + R_L} \Rightarrow 4 = \frac{10}{r + 2}$$

$$r = 0.5\Omega$$

Q) If 1A current is drawn from a cell, then its TPD is 20V but if 2A current is drawn from the cell, then its TPD is 10V. Find its EMF and internal resistance.

$$20 = E - I_1 r$$

$$20 = E - (1)r \quad \text{--- (I)}$$


$$10 = E - (2)r \quad \text{--- (II)}$$

$$\therefore 10 = E - 2(E - 20) \Rightarrow E - 2E + 40$$

$$\therefore \boxed{E = 30} \quad \therefore$$

$$r = E - 20 \Rightarrow 30 - 20 \Rightarrow \boxed{10}$$

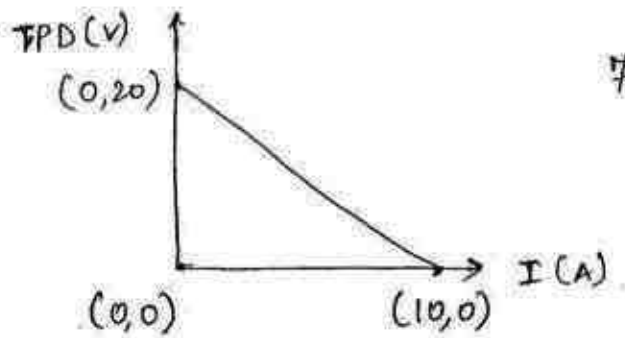2) A variable load is connected across the cell. and its graph for TPD versus I



Find its EMF and Internal resistance

$$\therefore \text{TPD} = E - Ix$$

$$20 = E - (0)x$$

$$\therefore E = 20V$$

$$\therefore \text{TPD} = E - Ix$$

$$0 = 20 - (10)x$$


$$\therefore x = 2\Omega$$

(OR)

$$\begin{array}{ccc} \text{TPD} & = & E - Ix \\ \downarrow & & \downarrow \\ y & & x \end{array}$$

$$(\because y = c - mx)$$

Q)

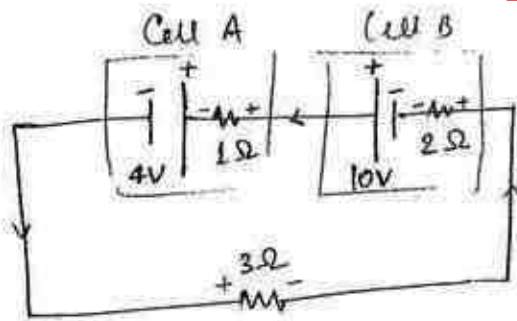

Find TPD of cell A and cell B


$$I = \frac{V_{\text{net}}}{R_{\text{net}}} = \frac{10 - 4}{1 + 2 + 3} = \frac{6}{6} = 1A$$

Cell A (charging)

$$\begin{aligned} \text{TPD}_A &= E + Ir \\ &= 4 + 1 \times 1 = 5V \end{aligned}$$

Cell B (discharging)
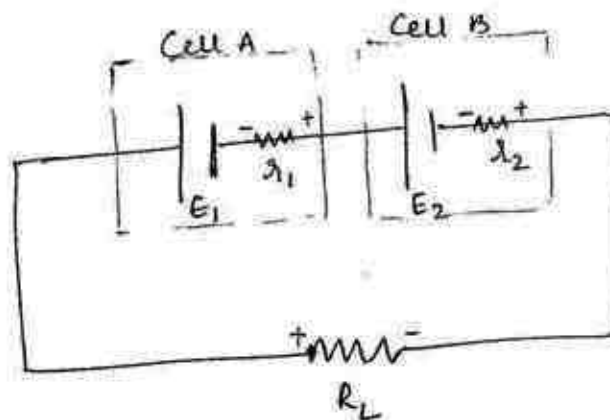
$$\begin{aligned} \text{TPD}_B &= E - Ir \\ &= 10 - 1 \times 2 = 8V \end{aligned}$$



If  $E_1 = E_2$  and TPD of cell A is zero then find value of  $R_L$  in terms of  $r_1$  and  $r_2$

$$\text{TPD} = E_1 - Ir_1$$

$$\therefore E = \frac{2E_1}{r_1 + r_2 + R_L}$$



$$\therefore E_1 = \text{TPD} + Ir_1$$

$$\therefore r_1 + r_2 + R_L = 2r_1$$

$$= 0 + \left( \frac{E_1 + E_2}{r_1 + r_2 + R_L} \right) r_1$$

$$\therefore \boxed{R_L = r_1 - r_2}$$

## Series combination of cells

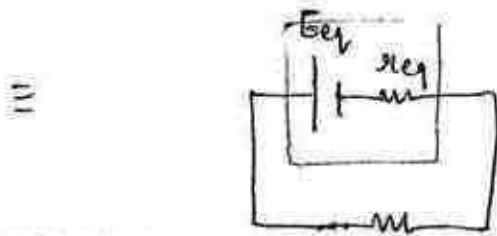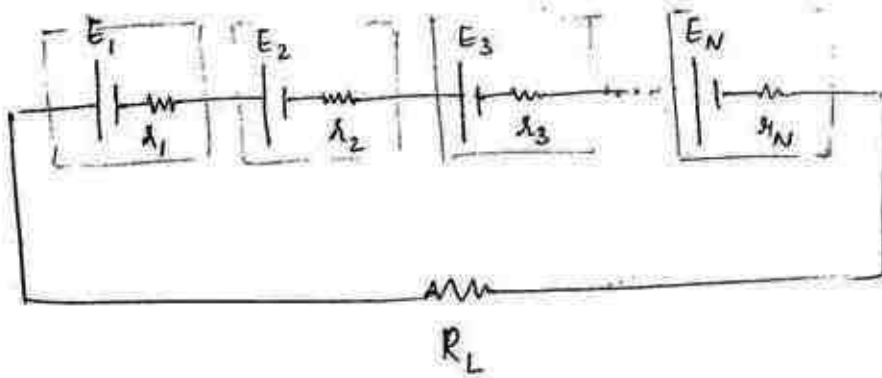

$$E_{eq} = E_1 + E_2 + \dots + E_N$$

$$r_{eq} = r_1 + r_2 + \dots + r_N$$

cells having same polarity have  $\oplus$  EMF and opposite polarity is taken as  $\ominus$  EMF

Q) There are 12 identical cells, connected in series with same polarity. This combination is connected across a load and current in the load is  $I$ . If polarity of  $N$  cells is reversed, then current in the load becomes  $\frac{2}{3}$  of  $I$ . Find value of  $N$ .

$$I = \frac{12E_1}{R_L + 12\Omega} \quad (1)$$

$$\frac{2I}{3} = \frac{(12-n)E_1 + (-nE_1)}{R_L + 12\Omega} = \frac{(12-2n)E_1}{R_L + 12\Omega} \quad (2)$$

$$\frac{(1)}{(1)} = \frac{(12-2n)E_1}{R_L + 12\Omega} = \frac{2I}{3}$$


$$\frac{12E_1}{R_L + 12\Omega} = I$$

$$\Rightarrow \frac{12-2n}{12} = \frac{2}{3} \quad \therefore 12-2n=8$$

$$\therefore \boxed{n=2}$$

Points to Remember:

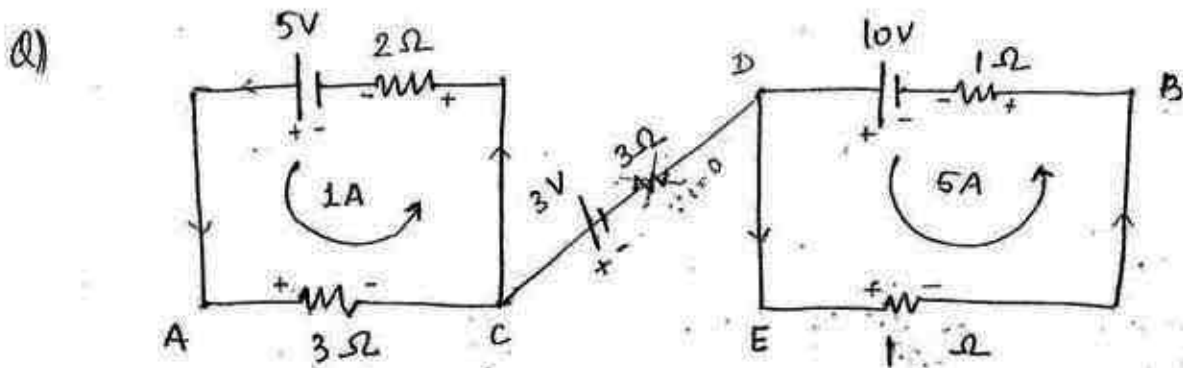If  $n$  cells are ~~removed~~ <sup>reversed</sup> then their will be diff. of  $2n$  cells in net EMF



find  $V_A - V_B$

Current in 1st loop =  $\frac{V}{R} = \frac{5}{5} = 1A$

2nd loop =  $\frac{V}{R} = \frac{10}{2} = 5A$

path ~~AB~~ ACDEB

$$V_A - 3 - 3 - 5 = V_B$$

$$\therefore V_A - V_B = 5 + 3 + 1 \\ = \boxed{11V}$$

Points to remember:


- > 2 loops are connected by a single wire then there will be no current in this wire.



- > ~~Its~~ current from the cell is zero but it has potential difference b/w its terminals.


Parallel combination of cell:

1) N identical cell:

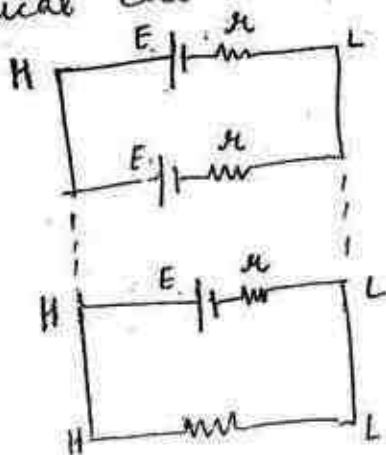

( $\because$  In parallel combination, potential remains same)

≡


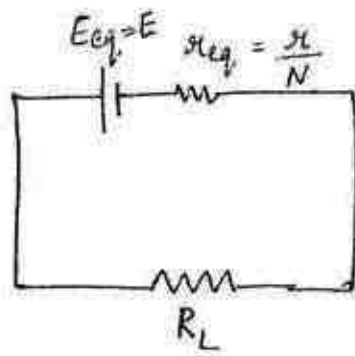


\* Efficiency ( $\eta$ ) =  $\frac{\text{output}}{\text{input}}$

i) Parallel combination of cell increases ampere hour rating of the group of cell. and decreases effective internal resistance. MAH  $\rightarrow$  milli Ampere h

ii) Effective EMF will not increase


Q)

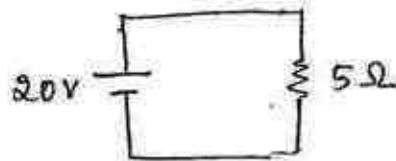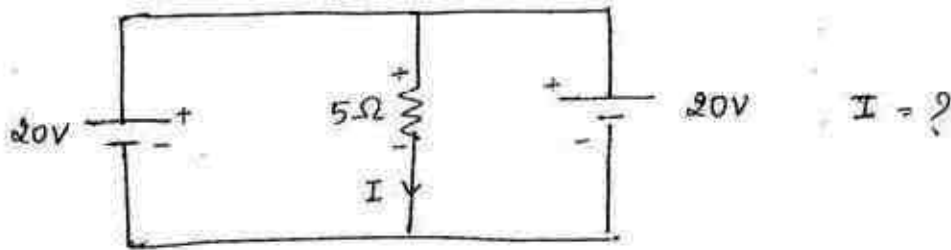

$\therefore I = \frac{V_{net}}{R_{net}} = \frac{20}{5} = 4$


( $\because$  cells are in || array)

Q)

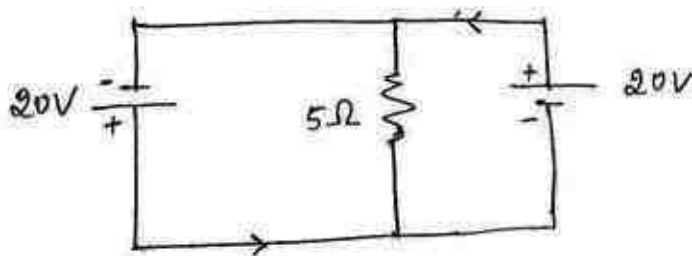


$I = 0$

Q)

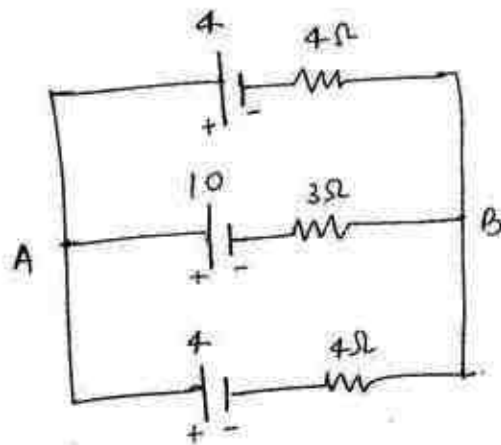

Calculate I  
in line AB.

≡

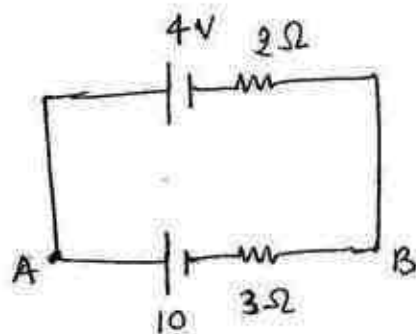

$$\therefore R_{\text{grouping}} = \frac{R}{2}$$


$$= \frac{4}{2} = 2\Omega$$

$$V_{\text{grouping}} = V \text{ (Parallel)}$$


$$\therefore I = \frac{V_{\text{net}}}{R_{\text{net}}} = \frac{10-4}{3+2} = \frac{6}{5} = 1.2 \text{ A}$$

\* Do not include the line AB in grouping of cell.  
(point of study)

Q)

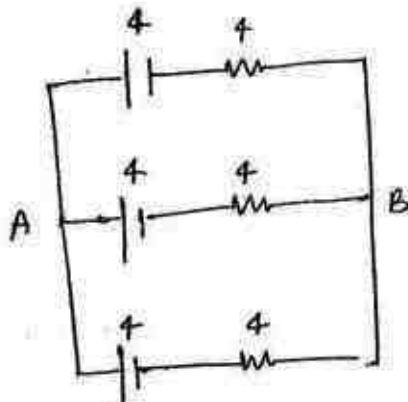


≡

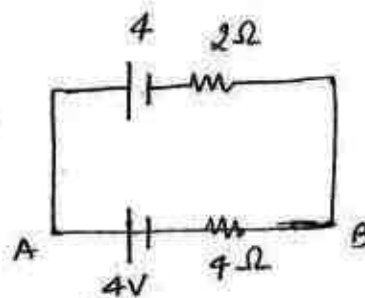


$$\therefore I = \frac{V_{\text{net}}}{R_{\text{net}}} = \frac{4-4}{6} = 0$$



Q)

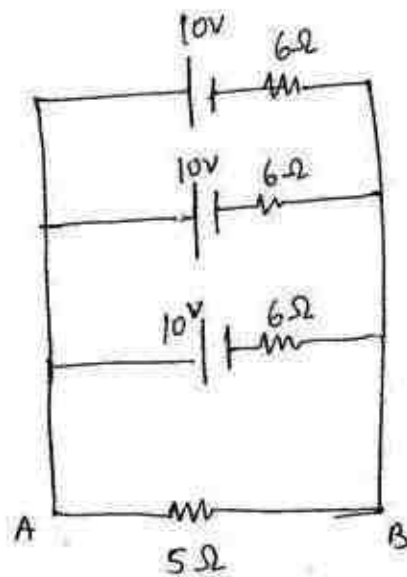


≡

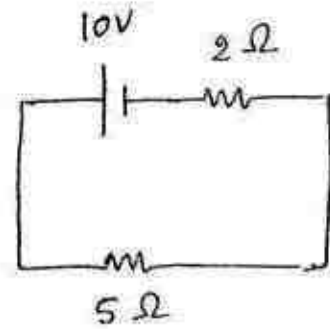

$$I = \frac{V_{\text{net}}}{R_{\text{net}}} = \frac{10}{2+5} = \frac{10}{7}$$

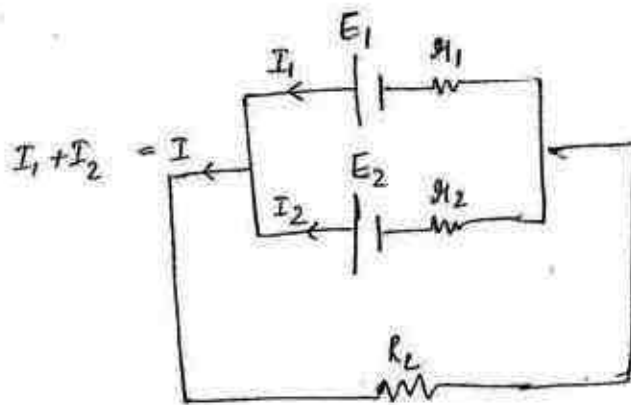ii) Two cells of different ( $E_1$  and  $r$ )



$$\therefore I = I_1 + I_2$$

$$\text{TPD} = E_1 - I_1 r_1 \quad \text{--- (I)}$$

$$\text{TPD} = E_2 - I_2 r_2 \quad \text{--- (II)}$$

[ $\because$  its in parallel]  
 $\therefore$  TPD are equal]

$$\therefore I = \left( \frac{E_1 - \text{TPD}}{r_1} \right) + \left( \frac{E_2 - \text{TPD}}{r_2} \right)$$


$$\text{TPD} \left( \frac{1}{r_1} + \frac{1}{r_2} \right) = \left( \frac{E_1}{r_1} + \frac{E_2}{r_2} \right) - I$$

$$\therefore \text{TPD} = \frac{\left( \frac{E_1}{r_1} + \frac{E_2}{r_2} \right)}{\left( \frac{1}{r_1} + \frac{1}{r_2} \right)} - \frac{I}{\left( \frac{1}{r_1} + \frac{1}{r_2} \right)}$$

for N cells:

$$* \therefore E_{eq} = \frac{\frac{E_1}{r_1} + \frac{E_2}{r_2} + \frac{E_3}{r_3} \dots \frac{E_N}{r_N}}{\left( \frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} \dots \frac{1}{r_N} \right)}$$
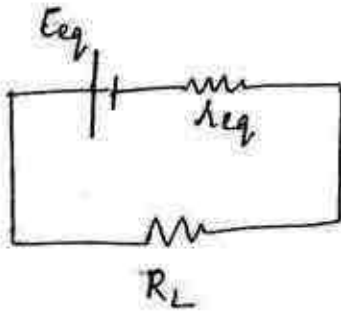
$$* r_{eq} = \frac{V \lambda(1)}{\lambda(1)}$$




N=2


$$E_{eq} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}$$

$$\therefore r_{eq} = \frac{r_1 r_2}{r_1 + r_2} \Rightarrow \frac{\text{product}}{\text{sum}}$$

Q)

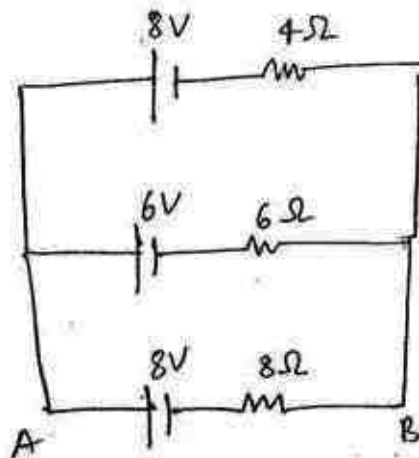

after grouping,

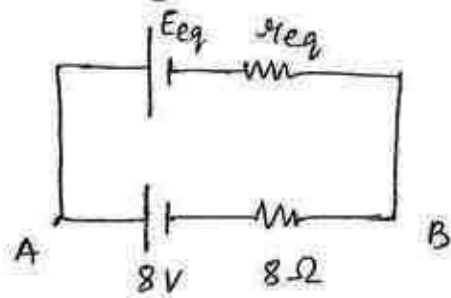

$$\text{here, } E_{eq} = \frac{E_1 R_2 + E_2 R_1}{R_1 + R_2}$$


$$= \frac{8 \times 6 + 6 \times 4}{6 + 4} = \frac{72}{10} = 7.2 \text{ V}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{6 \times 4}{6 + 4} = \frac{24}{10} = 2.4 \Omega$$

$$\therefore I = \frac{V_{net}}{R_{net}} = \frac{V_{eq}}{R_{eq}}$$

$$\Rightarrow \frac{8 - 7.2}{8 + 2.4} = \frac{0.8}{10.4} = \frac{1}{13}$$

Q)

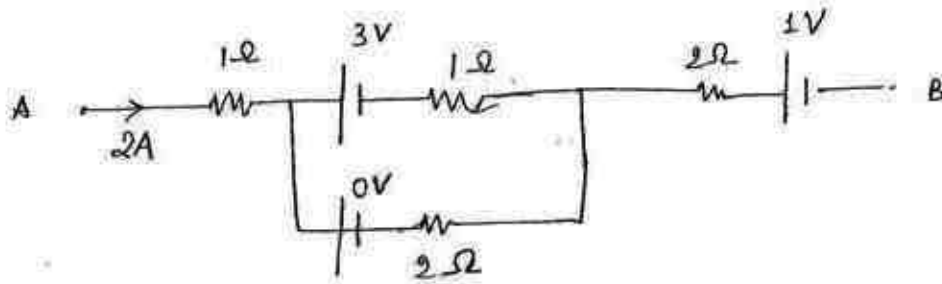


Find  $V_A - V_B$

$$E_{eq} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}$$

$$= \frac{3 \times 2 + 1 \times 0}{2 + 1} = \frac{6}{3} = 2V$$
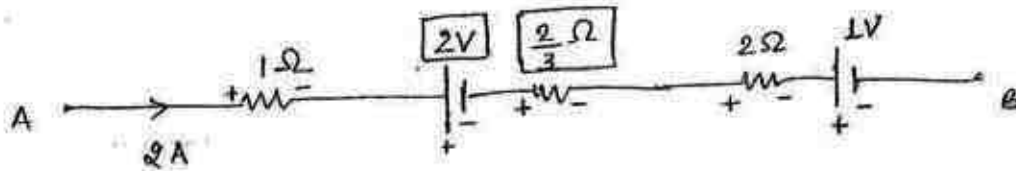
$$r_{eq} = \frac{2 \times 1}{2 + 1} = \frac{2}{3} \Omega$$



By KVL,


$$V_A - 2 - 2 - \frac{2}{3} \times 2 - 2 \times 2 - 1 = V_B$$

$$\therefore V_A - V_B = 2 + 2 + \frac{4}{3} + 4 + 1$$

$$= \frac{6 + 6 + 4 + 12 + 3}{3}$$

$$= \boxed{\frac{31}{3}}$$

AIPMT 2012  
Q)

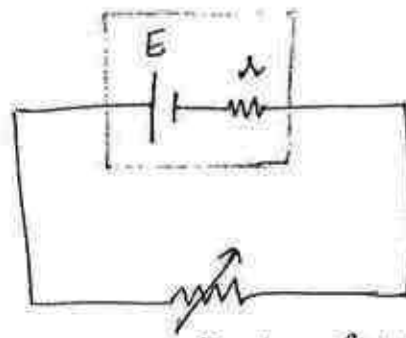

$R_L$  (variable)  
(0 to  $\infty$ )

Plot the graph b/w  $V$  across  $R_L$  and value of  $R_L$


$$V_L = IR_L$$

$$V_L = \left( \frac{E}{r + R_L} \right) R_L$$


$\therefore$  If  $R_L \ll r$

$$V_L = \left( \frac{E}{r} \right) R_L \quad \text{or} \quad V_L \propto R_L$$

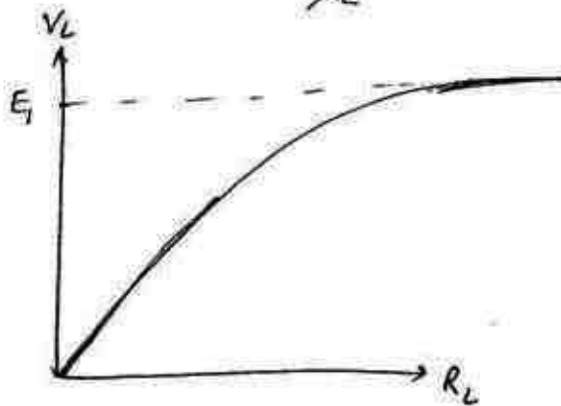If  $R_L \gg r$ ,  $V_L = \frac{E \times R_L}{R_L} \quad \therefore V_L = E$



## Electric power in the load $R_L$ :

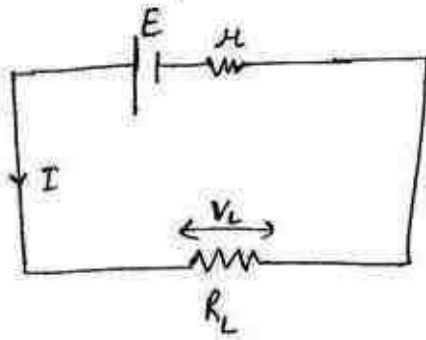

$$W = q(\Delta V)$$

$$W = q(V_L)$$

$$\therefore P_L = \frac{dW}{dt} = \frac{d(qV_L)}{dt}$$

$$\text{Energy} = P \times t = VI t$$

$$= V_L \frac{dq}{dt} = V_L (I)$$

$$= V_L \left( \frac{V_L}{R_L} \right) = \frac{V_L^2}{R_L} = I^2 R_L$$

$$\boxed{P_L = V_L I = \frac{V_L^2}{R} = I^2 R}$$


(Keep the corresponding values)

→ Power loss / Power gain / Power consumed / Power dissipated

Power in whole circuit:

$$P_{\text{total}} = \frac{E^2}{r + R_L} = I^2 (r + R_L) = E \cdot I$$

Q)

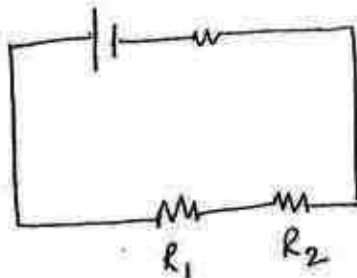


$I \Rightarrow$  same

$$\therefore P = I^2 R$$

$$P \propto R$$
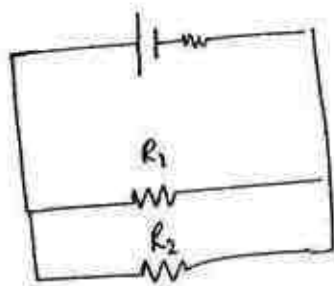
$$\therefore \frac{P_1}{P_2} = \frac{R_1}{R_2}$$




$V \Rightarrow$  same  
 $\therefore P = \frac{V^2}{R} \quad \therefore P \propto \frac{1}{R}$

$\therefore \frac{P_1}{P_2} = \frac{R_2}{R_1}$

calculate ratio of power dissipated in both cases

Q)

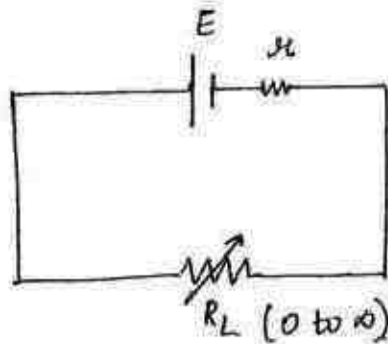

what should be the value of  $R_L$  such that power in the load will be maximum

$P_L = I^2 R_L$  [we cannot use  $\frac{d^2}{dx^2}$   $\therefore x$  is variable for every value whereas  $I$  is constant]

$= \left( \frac{E}{r + R_L} \right)^2 R_L = \underbrace{E^2}_{\text{constant}} \left[ \frac{R_L}{(r + R_L)^2} \right]$

For  $(P_L)_{\max} \quad \frac{dP_L}{dR_L} = 0$

$u = E R_L \quad v = (r + R_L)^2$

$\frac{dP_L}{dR_L} = E^2 \left[ \frac{(r + R_L)^2 \times \frac{dR_L}{dR_L} - R_L \times 2(r + R_L) \times \frac{d(r + R_L)}{dR_L}}{(r + R_L)^4} \right] = 0$

$(r + R_L) - 2R_L = 0$

$r - R_L = 0$

$R = r$

Points to remember:

i) Power in the load will be maximum if internal resistance and external resistance are equal and value of this maximum

$$\text{power } (P_L)_{\max} = \left( \frac{E}{r + R_L} \right)^2 R_L$$

$$= \left( \frac{E}{2r} \right)^2 r = \frac{E^2}{4r} \quad (\text{load})$$

→ internal resistance

ii) Power in the circuit will be maximum if variable resistance becomes zero


$$P_L = \frac{E^2}{r + R_L}$$

∴ If  $R_L = 0$  then  $P_T = \max$

$$(P_T)_{\max} = \frac{E^2}{r} \quad (\text{circuit})$$


→ internal resistance

Q1)

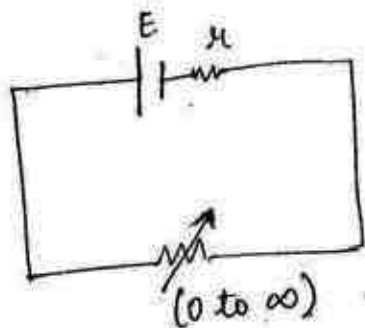

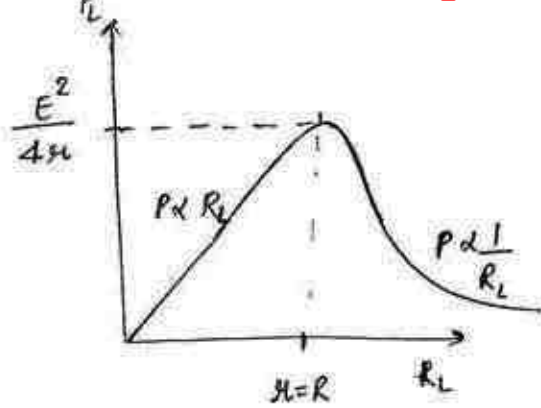Plot the graph.  
b/w 'Power in load' v/s  
value of  $R_L$





$$P_L = I^2 R_L$$

$$= \left( \frac{E}{R + R_L} \right)^2 R_L$$

i)  $R_L \ll R$

$$\therefore P_L = \left( \frac{E}{R} \right)^2 R_L \quad \therefore P_L \propto R_L \quad (\text{straight})$$


ii)  $R_L \gg R$

$$P_L = \left( \frac{E}{R_L} \right)^2 R_L = \frac{E^2}{R_L} \quad \therefore P_L \propto \frac{1}{R_L}$$

(Hyperbola)

Article : 6

Wheat Stone Bridge (W.S.B)

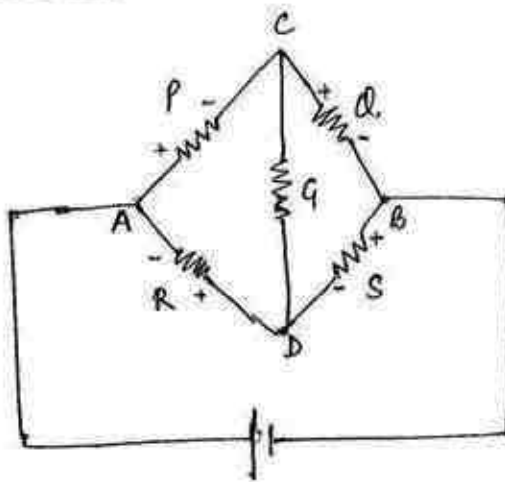

Points to remember :

i) If one diagonal is connected by middle arm (G) and second diagonal is to be connected or connected by battery, then network is called wheat stone bridge (WSB)

ii) If bridge is balanced, then  $V_C = V_D$  and  $\therefore$  current in middle arm will be zero so ammeter connected in middle arm will show zero deflection.

iii) If bridge is balanced, then

$$\frac{P}{Q} = \frac{R}{S} \quad \text{OR}$$

$$\frac{P}{R} = \frac{Q}{S}$$

iii) If pos<sup>n</sup> of battery and middle arm are interchanged in a balance WSB, then after change, bridge will be in balanced cond<sup>n</sup>

iv) If bridge is balanced the middle arm can

KVL in  $\Delta ACDA$


$$I_1 P = I_2 R \quad \text{--- (i)} \quad |loss| = |gain|$$

KVL in  $\Delta CBDC$

$$I_2 Q = I_1 S \quad \text{--- (ii)}$$

$$\text{(i) / (ii)} \quad \therefore \frac{P}{Q} = \frac{R}{S}$$

Q)

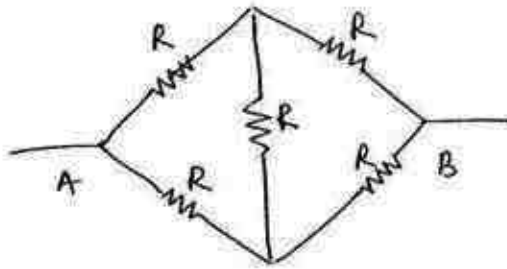


$$R_{AB} = \frac{2R}{2} = R$$

In balance WSB, result is independent of resistance of middle arm


Different form of WSB :

①

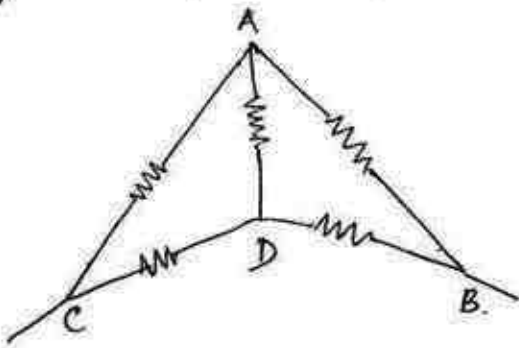


For CB, it is WSB  
and middle ~~arm~~ arm  $\rightarrow$  AD

2)

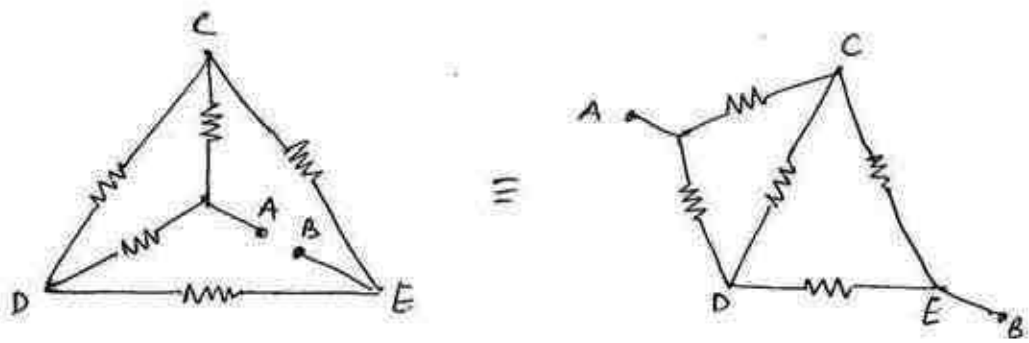


for AB, it is WSB and middle arm  $\Rightarrow$  CD

3)

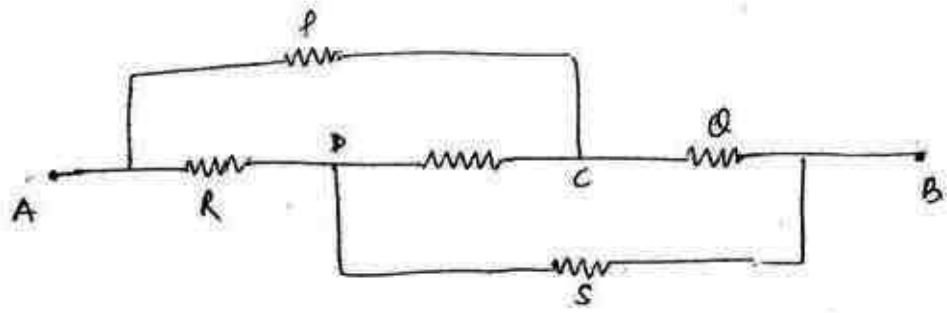


for AB, it is WSB and middle arm  $\Rightarrow$  CD

Q)

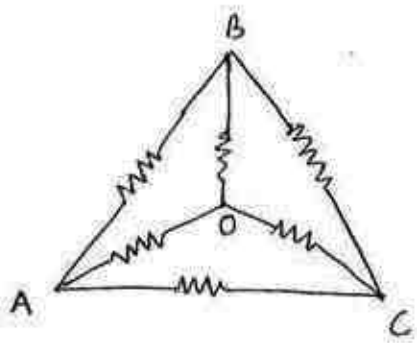


Each  $\rightarrow$  R  
find  $R_{AC}$   
 $R_{AO}$

$R_{AC} \Rightarrow$

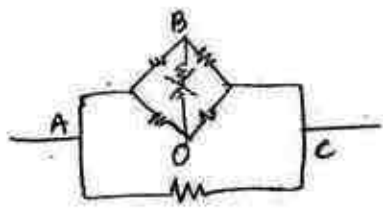


~~R~~  $\frac{R}{2}$

$R_{AO} \Rightarrow$

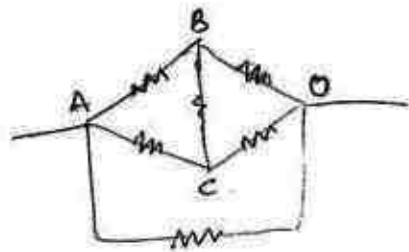


$\frac{R}{2}$

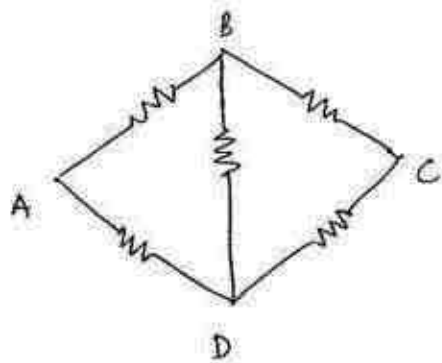

Each R

Find  $R_{AB}$ ,  $R_{AC}$ ,  $R_{AD}$ ,  $R_B$


i)  $R_{AB} \Rightarrow$

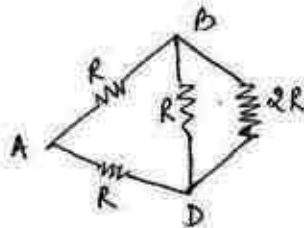

From B to D

$$(R_{net})_{BD} \Rightarrow \frac{R \times 2R}{R + 2R} = \frac{2R}{3}$$

( $\because$  its in parallel)

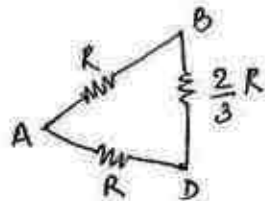

$$(R_{net})_{AB} \Rightarrow \frac{2R}{3} + R = \frac{5R}{3}$$

$$\therefore (R_{net})_{AB} = \frac{\frac{5R}{3} \times R}{\frac{5R}{3} + R} = \frac{\frac{5R^2}{3}}{\frac{8R}{3}} = \frac{5R}{8}$$


ii)  $R_{AC} \Rightarrow$



$$\frac{2R}{2} = R$$

iii)  $R_{AD} \Rightarrow \frac{5R}{8}$


iv)  $R_{BD} \Rightarrow$

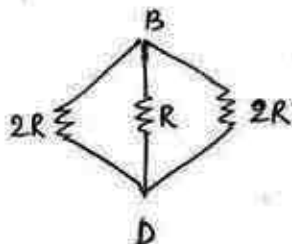


$$\frac{1}{R_{net}} \Rightarrow \frac{1}{2R} + \frac{1}{R} + \frac{1}{2R}$$

$$\frac{1 + 1 + 2}{2R} = \frac{4}{2R} = \frac{2}{R}$$
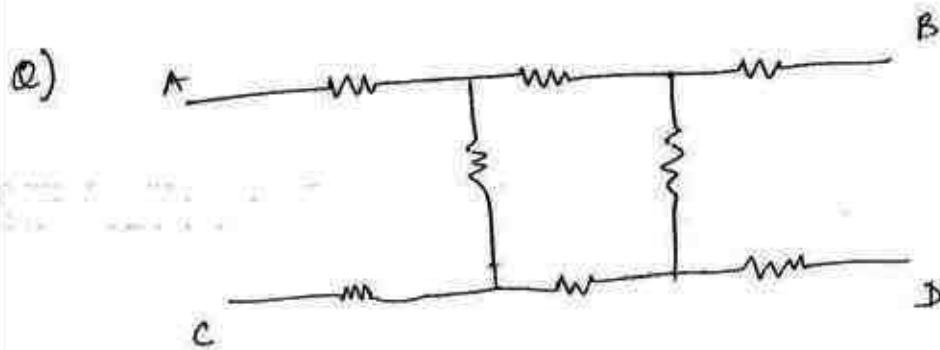
$$\therefore R_{net} \Rightarrow \frac{R}{2}$$



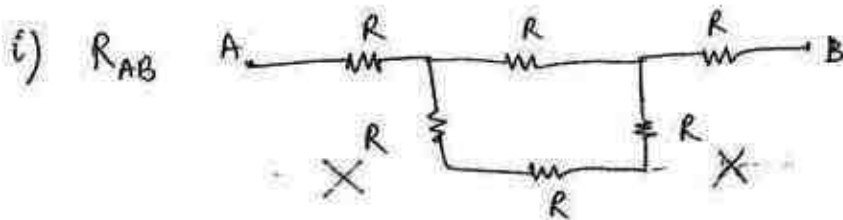Each  $\rightarrow R$   
 Find  $R_{AB}$   
 $R_{AC}$   
 $R_{AD}$




$\therefore R_{AB} = \because 3R$  and  $R$  are in ||al

$$\therefore \frac{3R \times R}{3R + R} = \frac{3R}{4}$$

$$\text{For } AB = \frac{3R}{4} + R + R = \frac{11}{4} R$$


ii)

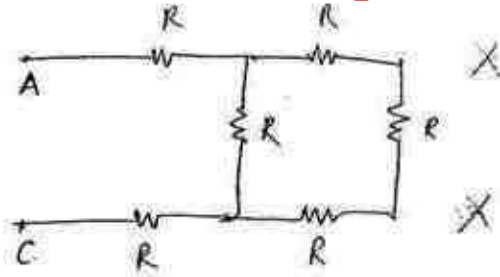


$$R_{AC} = \frac{3R \times R}{3R + R} \Rightarrow \frac{3R}{4}$$

$$\therefore \text{For } AC = \frac{3R}{4} + R + R = \frac{11R}{4}$$

iii)


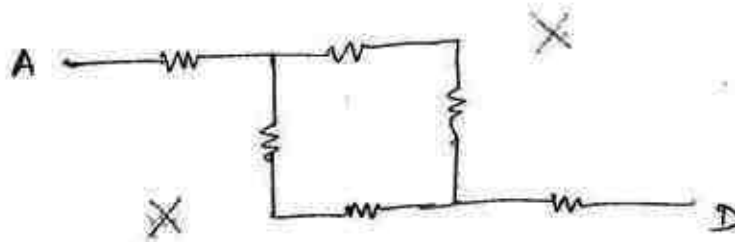


$\therefore$

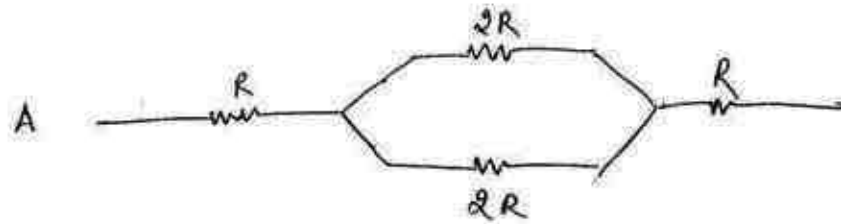

$$\Rightarrow 3R$$

Q)

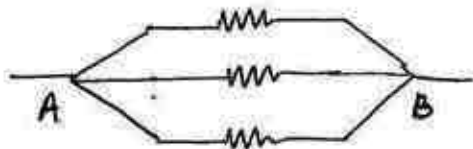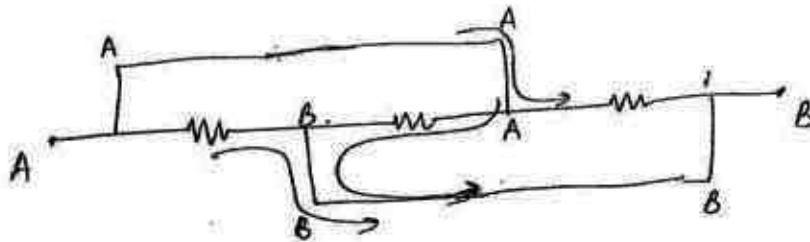


$$\frac{1}{R_{net}} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R}$$

$$\frac{1}{R_{net}} = \frac{3}{R}$$

$$\therefore R_{net} = R$$

Q1)

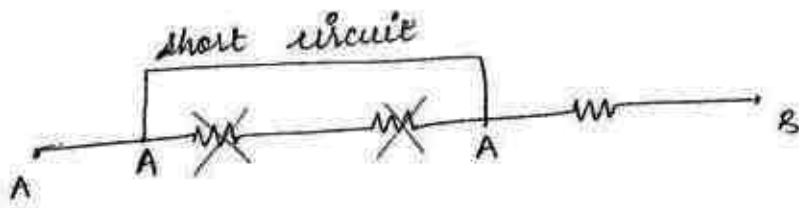


Find  $R_{AB}$

$$\therefore R_{AB} = R$$


"Using equipotential method"

Q2)

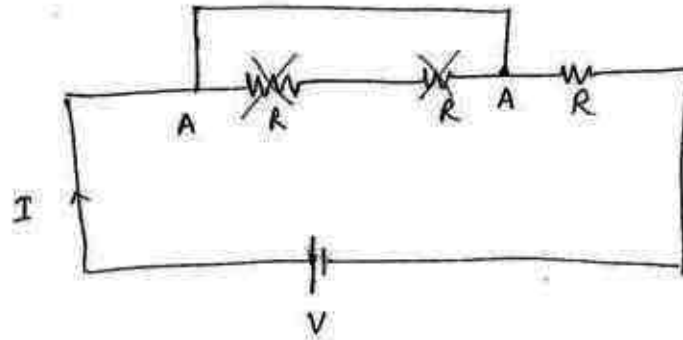


$$\therefore I = \frac{V}{R} \quad (\because R_{net} = R)$$

Q3)

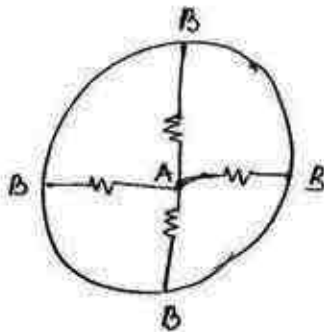

Each  $R$

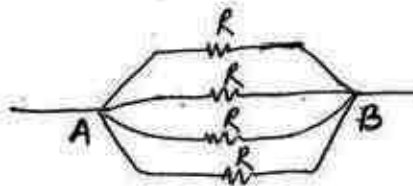


$$\frac{1}{R_{net}} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \frac{1}{R}$$


$$\frac{1}{R_{net}} = \frac{4}{R} \quad \therefore R_{net} = \frac{R}{4}$$



Q)


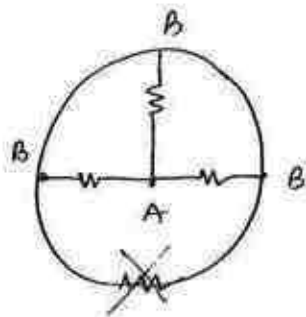


Each R  
Find AB

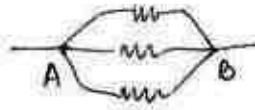



$$\therefore R_{AB} = \frac{R}{3}$$

Q)

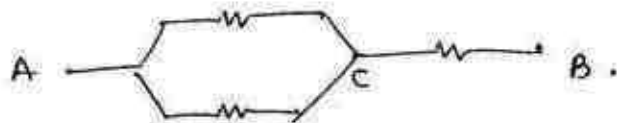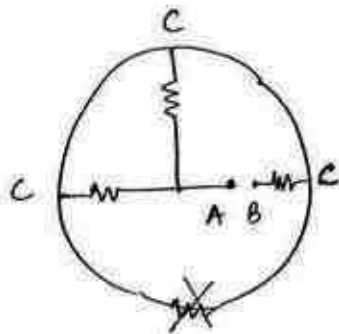

$$\therefore R_{AB} = \frac{R}{2} + R = \frac{3R}{2}$$



Q)

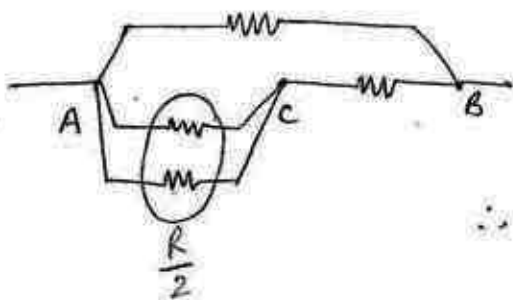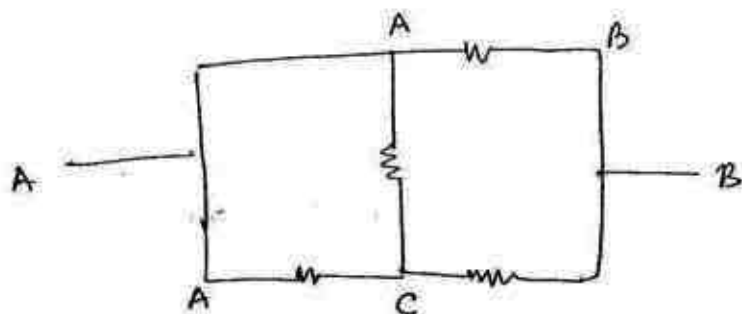

$$\Rightarrow \frac{R}{2} + R \Rightarrow \frac{3R}{2}$$

$$\therefore R_{net} \Rightarrow \frac{\frac{3R}{2} \times R}{\frac{3R}{2} + R} \Rightarrow \frac{3R}{5}$$

Q)

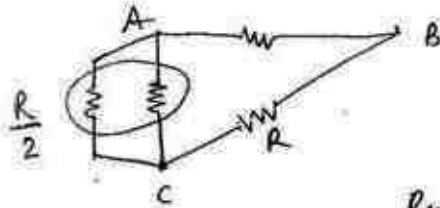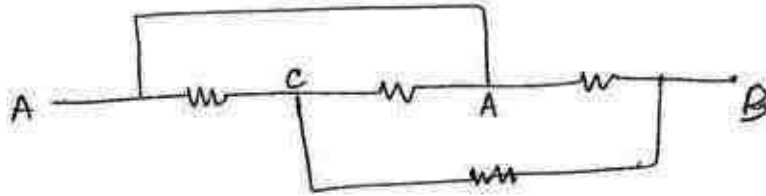


$$\frac{R}{2} + R = \frac{3R}{2} (\because \text{series})$$


$$R_{net} = \frac{\frac{3R}{2} \times R}{\frac{3R}{2} + R} = \frac{3R}{5}$$

\* Equipotential method can be used if few resistance or few branches are short circuiting

Q)

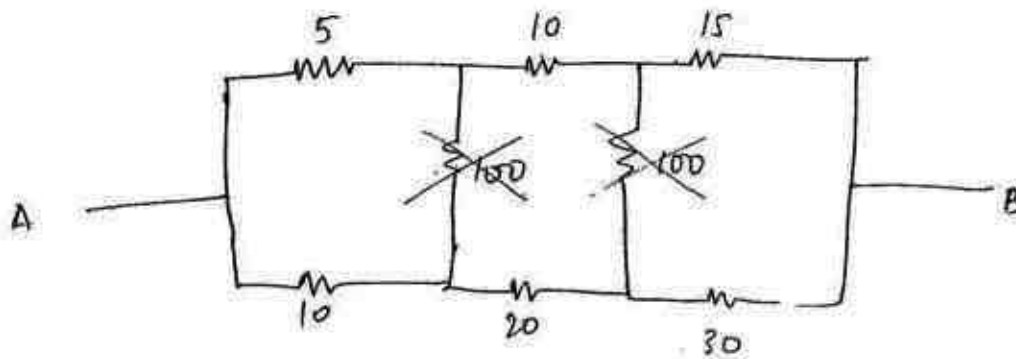

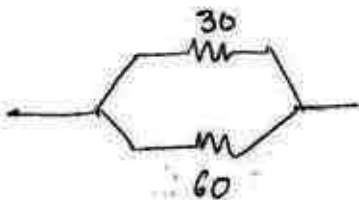$\therefore$  It is extension of balanced WSB.




$$\frac{1}{R_{net}} = \frac{1}{30} + \frac{1}{60}$$

$$= \frac{6 + 3}{180} = \frac{9}{180} = \frac{1}{20}$$

$$\therefore R_{net} = 20$$


Q) \*

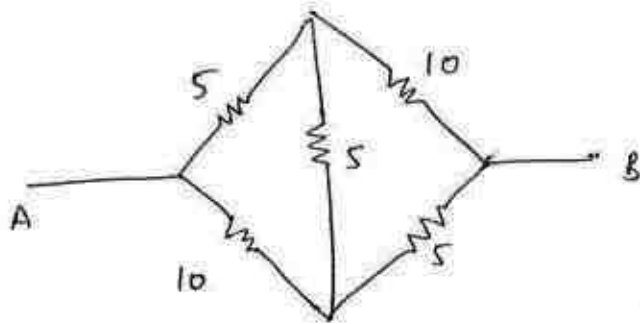

Find  $R_{AB}$

(Imbalanced w.r. B)

\*  $|gain| = |loss|$

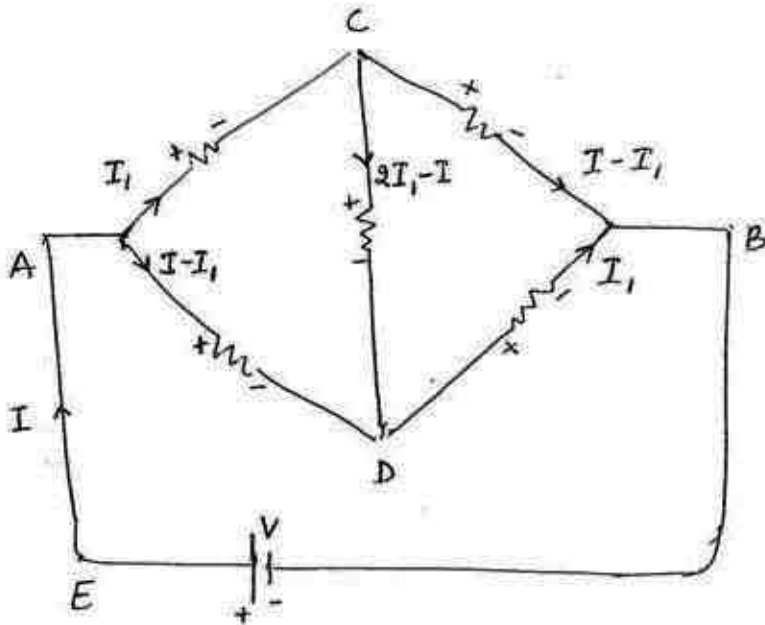

By KVL, in ACBEA

$$V_A - 5(I_1) - (I - I_1)10 + V = V_A$$

$$\therefore V = (I - I_1)10 + 5I_1$$

$$\therefore V = 10I - 10I_1 + 5I_1 = 10I - 5I_1 \quad \text{--- (I)}$$

By KVL in ACDA

$$V_A - 5(I_1) - (2I_1 - I)5 + (I - I_1)10 = V_A$$

$$\therefore -5I_1 - 10I_1 + 5I + 10I - 10I_1 = 0$$


$$\therefore 15I = 25I_1 \quad \Rightarrow \quad 3I = 5I_1 \quad \text{--- (II)}$$

from (I) and (II)

$$10I - 3I = V \quad \therefore V = 7I$$

$$\therefore R_{eq} = \frac{V}{I} = \frac{7I}{I} = \boxed{7\Omega}$$

Q) short  
circuit

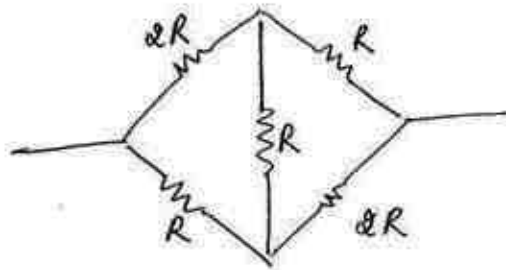

$$\therefore R_{AB} = \frac{7R}{5}$$

→ add all the resistance and then divide it by no. of resistance


### Symmetrical line method


If there is a line which bisects the given network into two equal sections & then all the points on this line have same potential. so we can remove wires and junctions lying on this symmetrical line.

Points to remember




Symmetrical line is not allowed to pass through the terminals given for study

Method of removing junction

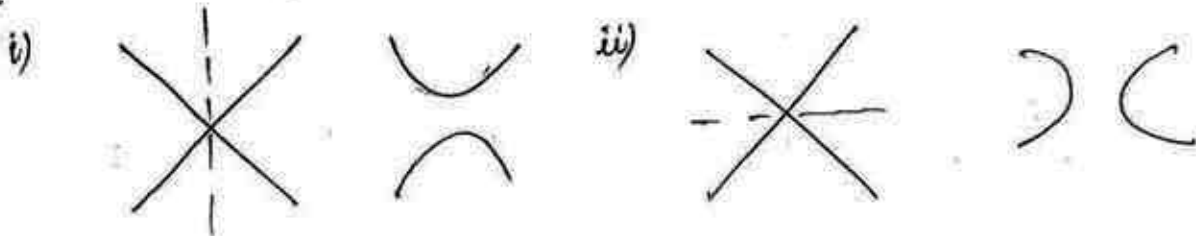


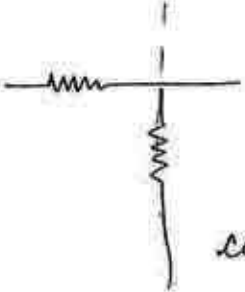
>  can't be removed  $\Rightarrow$  (across the line)  
 can be removed  $\Rightarrow$  (along the line)


Q)

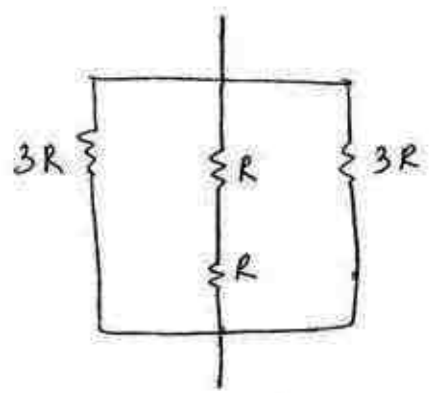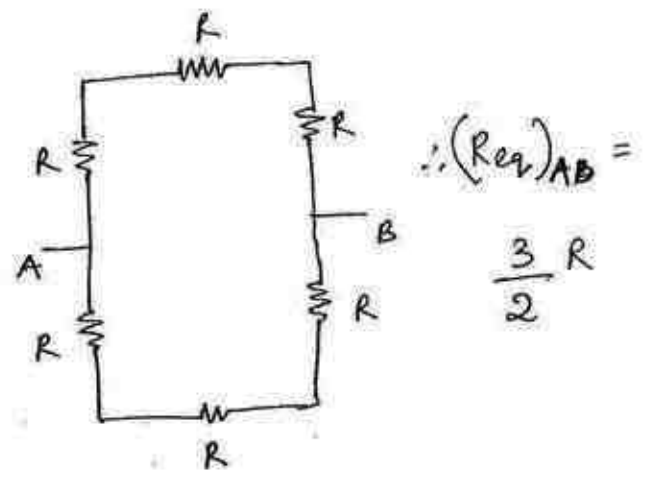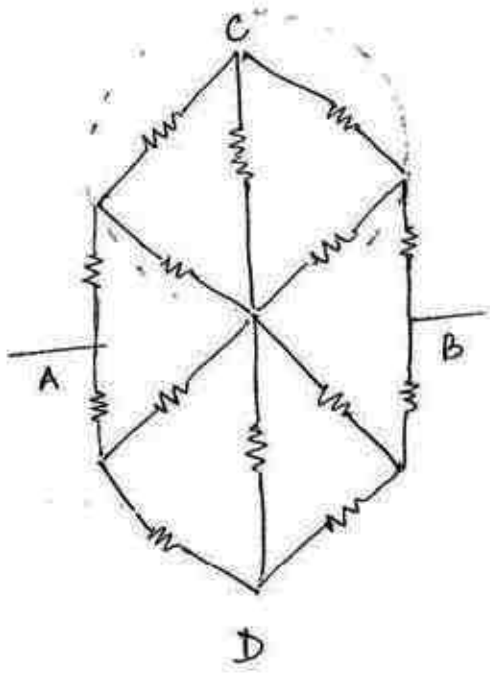



$\therefore (R_{eq})_{CD} = \frac{\frac{3R}{2} \times 2R}{\frac{3R}{2} + 2R}$   
 $= \frac{6R}{7}$

Q)

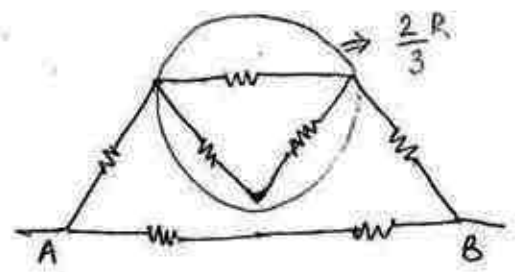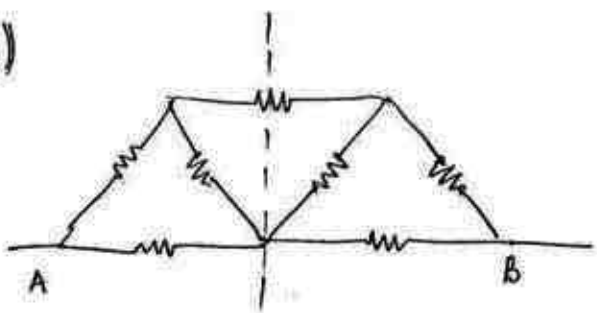

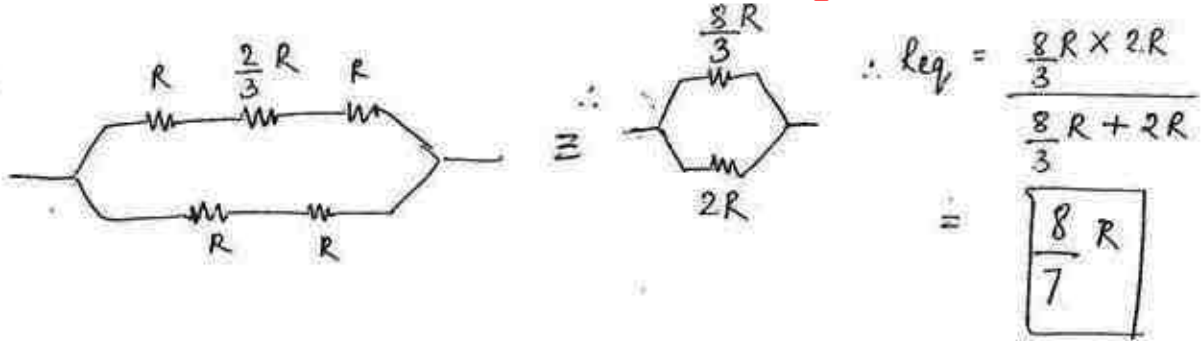


Q1

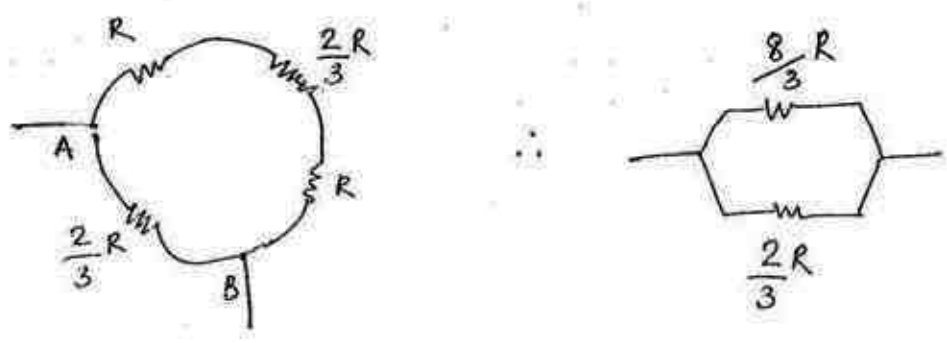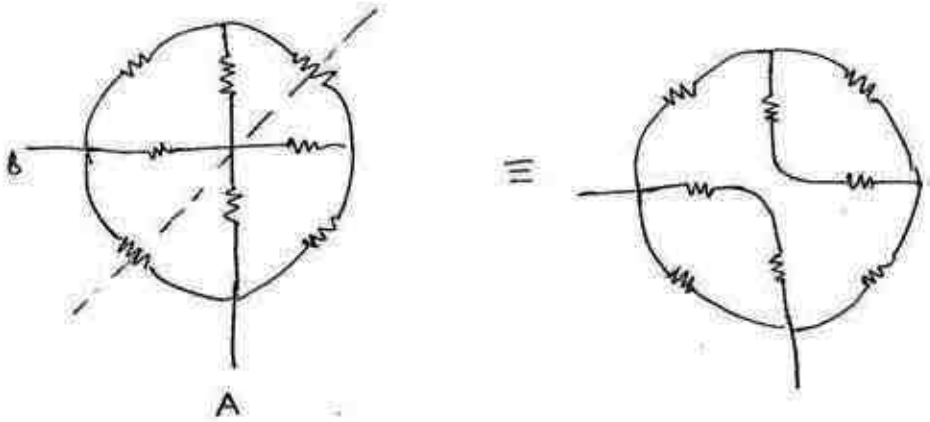


$$\begin{aligned}
 \therefore R_{eq} &= \frac{8R \times 2R}{8R + 2R} \\
 &= \frac{16R^2}{9} \times \frac{3}{10R} = \boxed{\frac{8R}{15}}
 \end{aligned}$$

# Ladder Network

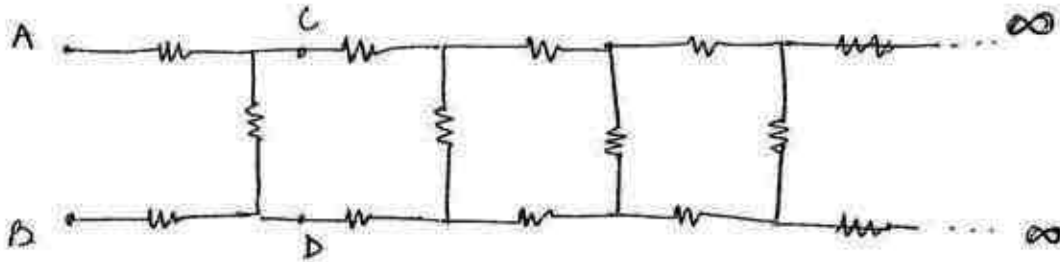

Each  $\rightarrow R$   
find  $R_{AB}$

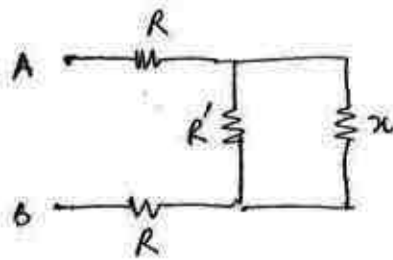Let  $R_{AB} = x \quad \therefore \text{so } R_{CD} = x \quad (\because \infty - 1 = \infty)$



for competition  $\left[ \begin{array}{l} \text{R} \\ \text{R} \\ \text{R} \end{array} \right] \therefore R_{net} = 2R = \frac{R \times 2R}{R + 2R} \approx \boxed{2.15 R}$   
 $\therefore$  we can ignore other resistances which contribute almost negligible

$$R_{AB} = R + R' + R = 2R + R'$$

$$\therefore x = 2R + \frac{Rx}{R+x} \Rightarrow x(R+x) = 2R(R+x) + Rx$$

$$xR + x^2 = 2R^2 + 2Rx + Rx$$

$$\therefore x^2 - 2Rx - 2R^2 = 0$$

$$\begin{cases} a = 1 \\ b = -2R \\ c = -2R^2 \end{cases}$$


$$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$= \frac{2R \pm \sqrt{4R^2 - 4(1)(-2R^2)}}{2 \times 1}$$


$$= R(1 \pm \sqrt{3})$$

$$= \underline{2R \pm 2\sqrt{3}R}$$


$$\therefore \boxed{x = 2.732R}$$

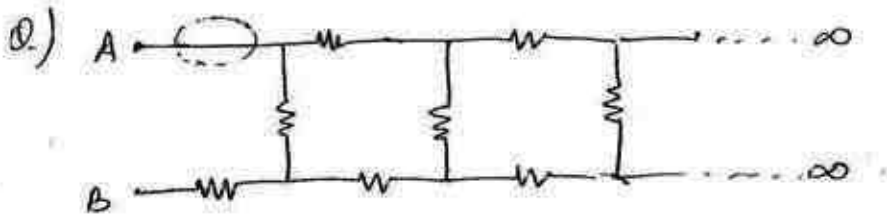
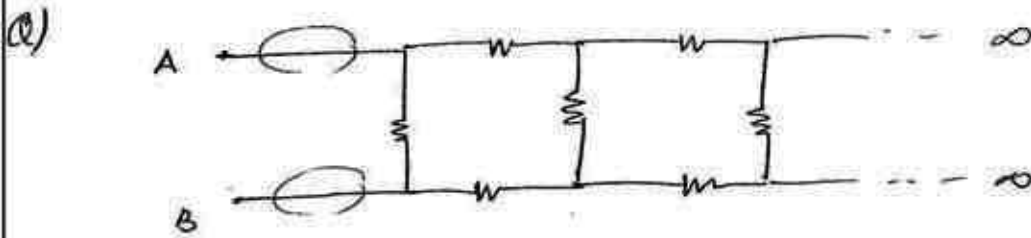
$$\therefore R_{AB} = \sqrt{3}R = \boxed{1.732R}$$



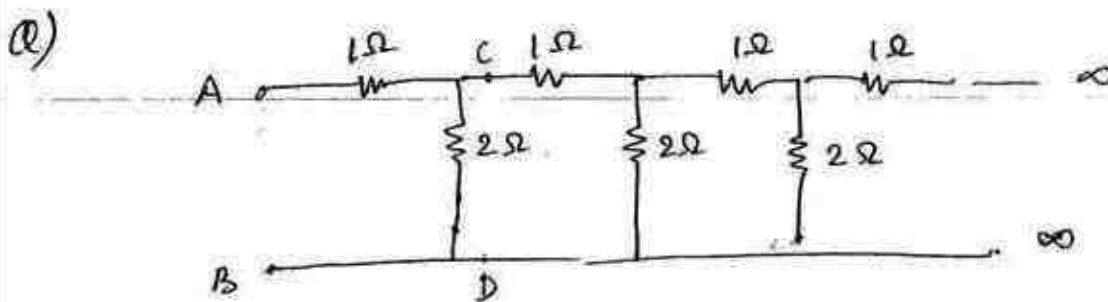
$$\therefore R_{AB} = (\sqrt{3}-1)R = \boxed{0.732R}$$



let  $R_{AB} = x$

$\therefore$  so  $R_{CD} = x$

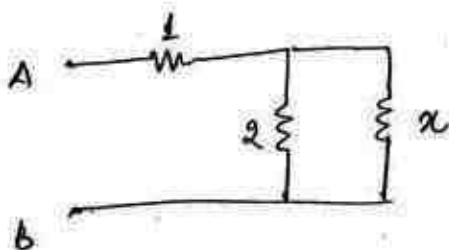

$$\therefore x = 1 + \frac{2x}{2+x}$$

$$x^2 + 2x = 2 + x + 2x$$

$$\therefore x^2 - x - 2 = 0$$

$$(x-2)(x+1) = 0$$

$$\therefore \boxed{x=2}, x=-1$$




# Galvanometer / Voltmeter / Ammeter



Points to remember:


> Moving coil meters are based on magnetic effect of current

> magnetic torque,  $\tau \propto I$   
 $\therefore$  deflection i.e.  $\phi \propto I$

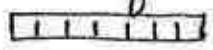so that scale of these meters are uniform  
 (equal distribution) 

> Ammeter should have negligible resistance and voltmeter should have very high resistance
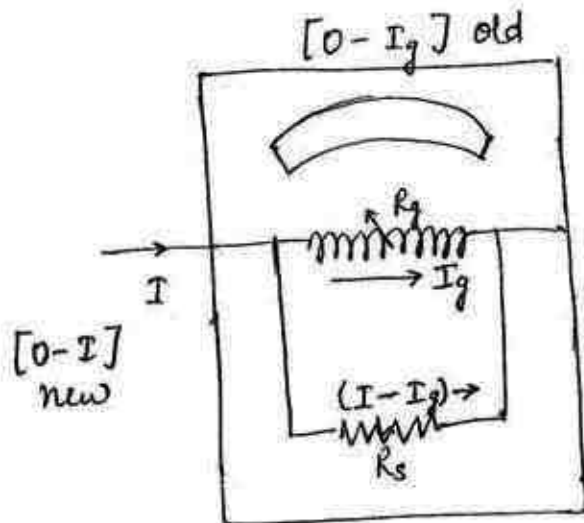
> Resistance of ideal ammeter is zero and ideal voltmeter is infinite



here,  $R_s$  = shunt resistance or small resistance

$$I_g R_g = (I - I_g) R_s$$

previous range
new range

Ammeter  
 (more delicate)

Q) Resistance of a galvanometer is  $G$ , we want to ↑ its current range  $n$  times of initial value. Find required value of shunt resistance

$$\therefore R_g \underset{\substack{\downarrow \\ \text{previous} \\ \text{range}}}{I_g} = \underset{\substack{\downarrow \\ \text{new} \\ \text{range}}}{(I - I_g)} R_s$$

$$I_g \times G = (nI_g - I_g) R_s$$

$$\cancel{I_g} \times G = \cancel{I_g} (n-1) R_s$$


$$\therefore R_s = \left( \frac{G}{n-1} \right)$$

A resistance of low value is connected in parallel with the coil of  $-G-$  so effective resistance of  $-A-$  can be decreased. This parallel resistance is called shunt resistance

→ ~~the~~ with the ~~the~~ help of shunt resistance, desired current range can be achieved

$I_g$   $\left\{ \begin{array}{l} \rightarrow \text{max allowed current} \\ \rightarrow \text{current range} \\ \rightarrow \text{full scale deflection current} \end{array} \right.$

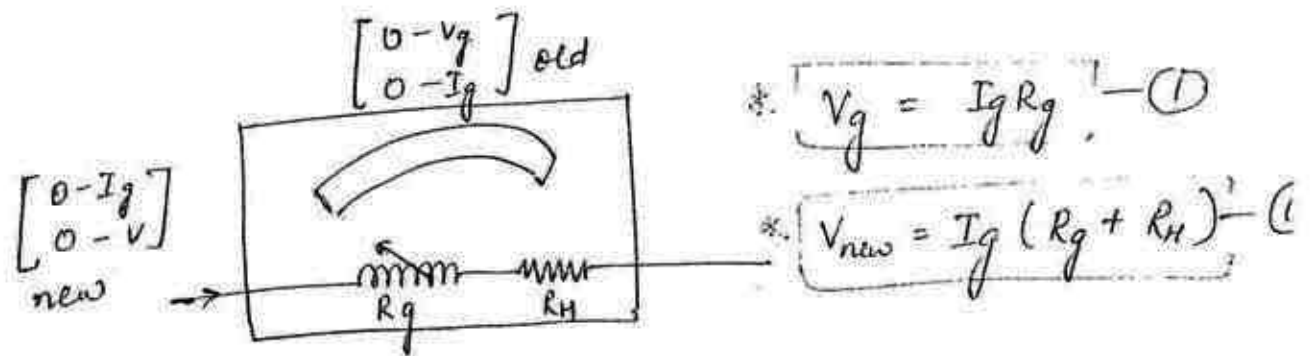Conversion of  $\text{G}$  into  $\text{V}$



Note:

A resistance of high value is connected in series with the coil of  $\text{G}$  to  $\uparrow$  effective resistance

$\gg$  This additional resistance will change voltage range of meter

Q) Resistance of a galvanometer is  $\text{G}$  - we want to  $\uparrow$  its voltage range upto  $n$  times of initial. Find required value of series resistance

$$\therefore V_g = I_g R_g \quad \text{--- (1)} \quad \text{and} \quad I_g R_g = I_g (R_g + R_H)$$

$$\therefore n I_g R_g = I_g (R_g + R_H)$$

$$\therefore R_g (n-1) = R_H$$

$$\therefore R_H = G (n-1)$$

Q1) Value of  $R_g$  is  $30\ \Omega$  and its current range is  $1\text{mA}$ . We want to read max.  $30\text{V}$  with this meter. Find required series resistance.

$$\therefore V = I_g (R_g + R_H)$$

$$30 = 10^{-3} (30 + R_H)$$

$$\therefore R_H = \frac{30 - (30 \times 10^{-3})}{10^{-3}} = 29970\ \Omega$$

Q2) Voltage range of a meter is  $10\text{V}$ . and its resistance is  $10\ \Omega$ . we want to read  $100\text{V}$  with this meter. calculate value of addition series resistance

$$\therefore V_g = I_g R_g$$

$$\therefore I_g = \frac{V_g}{R_g} = \frac{10}{10} = 1\text{A}$$

$$\therefore V = I_g (R_g + R_H)$$

$$\therefore 100 = 1 (10 + R_H)$$

$$\therefore R_H = 100 - 10 = 90\ \Omega$$


Q3)  $R_g = 100\ \Omega$  and its current range is  $10^{-5}\text{A}$ . we want to read  $1\text{A}$  with this meter. Find approx value of shunt resistance

$$\therefore I_g R_g = (I - I_g) R_s$$

$$\therefore 10^{-5} \times 100 = (1 - 10^{-5}) R_s$$

$$\therefore R_s = \frac{10^{-5} \times 10^2}{1 - 10^{-5}} = 10^{-3}\ \Omega$$

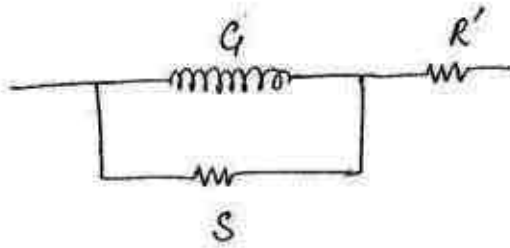\*Q) Resistance of a galvanometer is  $G$ . It is shunted by a resistance  $S$ . ~~This meter~~ A series resistance is connected with this meter. What should be value of series resistance so main current in the meter remains same.



$$\therefore \frac{G \times S}{G + S} + R' = G$$

$$\therefore R' = G - \frac{GS}{G + S}$$

$$= \frac{G^2}{G + S}$$

Same current  
 $\therefore I = \frac{V}{R}$  constant for a circuit  
 $\therefore R$  should be same

\*Q)  $R_g = 10 \Omega$ , no of divisions in the scale of meter is 50. and 1A current is required for deflection of one division. we want to read 1KV with is meter. Find value of series resistance  $\because 1 \text{ division} = 1A \therefore 50 \text{ division} = 50A$


$$\therefore V = I_g (R_g + R_H)$$

$$1000 = 50 (10 + R_H)$$

$$\therefore R_H = \frac{1000 - 500}{50} = 10 \Omega$$
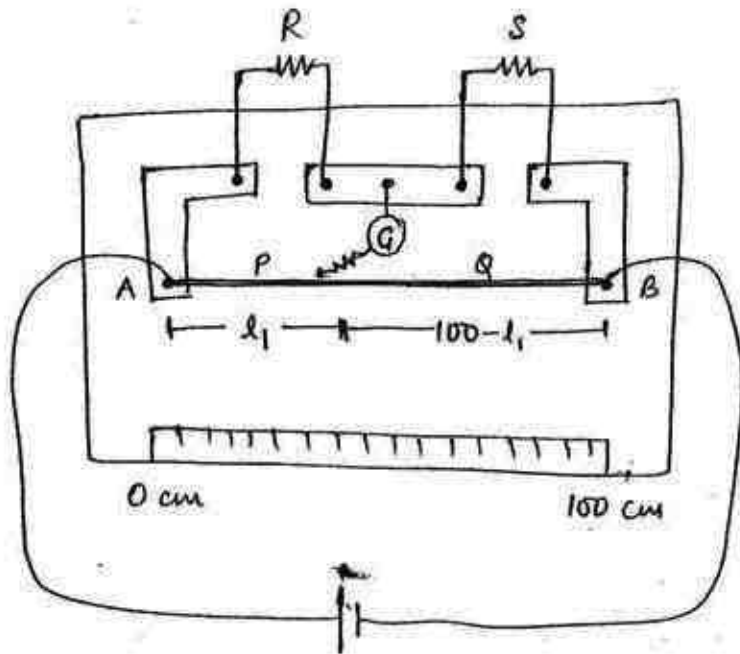
## Meter Bridge:

→ based on principle of balanced wheat stone bridge:



For null point:

$$\frac{P}{Q} = \frac{R}{S}$$

$$\frac{l_1}{100 - l_1} = \frac{R}{S}$$

Points to remember

- length of AB wire is always 100 cm (1m)
- position of null point is independent of area of cross section of AB wire.

Q) In the given diagram  $R = 110 \Omega$  and distance of null point from B is 45 cm. Find the value of S

$$\therefore \frac{P}{Q} = \frac{R}{S}$$

$$\frac{l_1}{100 - l_1} = \frac{R}{S} \Rightarrow \frac{45}{100 - 45} = \frac{110}{S}$$

$$\frac{55}{45} = \frac{110}{S} \quad \therefore S = \frac{110 \times 45}{55} = 90 \Omega$$

Q1) In the given diagram  $R:S \Rightarrow 1:4$  and distance of null point from A is  $l_1$ . If R and S are interchanged, then distance of null point from A is  $l_2$ , find  $l_2 - l_1$

$$\therefore R:S = 1:4 = \frac{1}{5} \times 100 : \frac{4}{5} \times 100 \Rightarrow 20:80$$

$$\therefore 20:80 \Rightarrow l_1 = 100 - l_1$$

$$\text{now, } 80:20 \Rightarrow l_2 = 100 - l_2$$

$$\therefore l_2 = 80, \quad l_1 = 20$$

$$\therefore l_2 - l_1 = 60$$

Q2) In the given diagram, ~~dist~~ pos<sup>n</sup> of null point is at midpoint of A and B. Now resistance R is shunted by  $10 \Omega$  and null point shift by 20 cm. Find the value of shunted resistor

$$R = S$$

$$\frac{R'}{S} = \frac{30}{70}$$


$$\left( \frac{10R}{10+R} \right) \frac{1}{R} = \frac{3}{7} \Rightarrow 70 = 30 + 3R$$

$$\therefore R = \frac{40}{3} \Omega$$


Article : 7

# Potentiometer (P.M) \*\*

used to measure emf

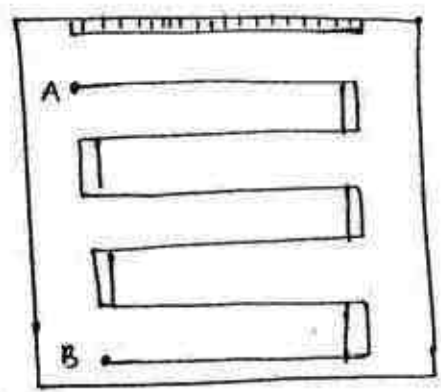

Points to remember:

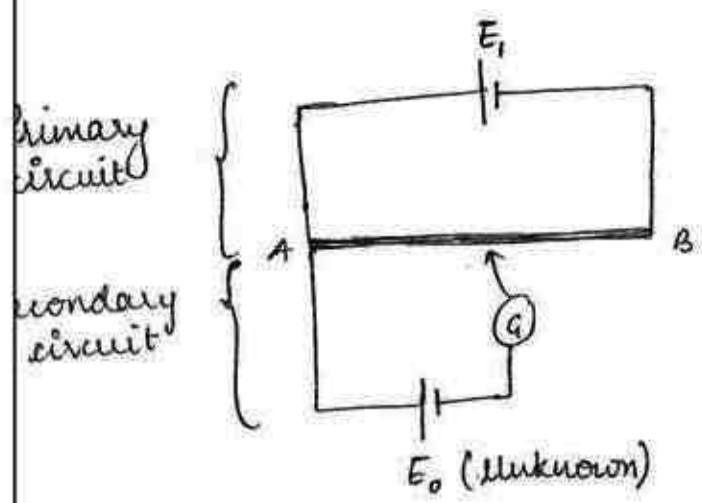

Its working is based on null deflection, it means it doesn't draw any current from secondary circuit so it can be used as an ideal voltmeter and ideal ammeter

Potential gradient on the wire is potential per unit length,

$$\phi = \frac{V_w}{L_w} = \frac{\text{voltage of wire}}{\text{length of wire}}$$



⇒ sensitivity of potentiometer is inversely proportional to  $\phi$

$$\text{sensitivity} \propto \frac{1}{\phi} \propto \frac{L_w}{V_w}$$


⇒ By increasing length of wire, sensitivity can be increased without changing its range that's why its length is kept very long.

⇒ If null deflection is not obtained on the wire, then there may be two possibilities.

↳ Potential of unknown cell is more than voltage of the wire.

↳ same polarity of all cells is not connected at starting terminal of AB wire.

⇒ Actual Potentiometer

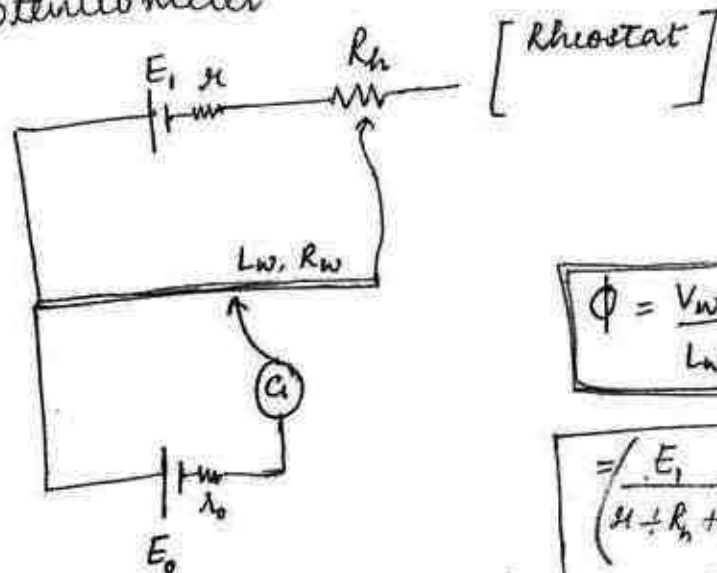


$$\phi = \frac{V_w}{L_w} = \frac{I_w R_w}{L_w}$$

$$= \left( \frac{E_1}{r_1 + R_h + R_w} \right) \frac{R_w}{L_w}$$

Q) In the given diagram, calculate ratio of  $\phi_{\min}$  and  $\phi_{\max}$
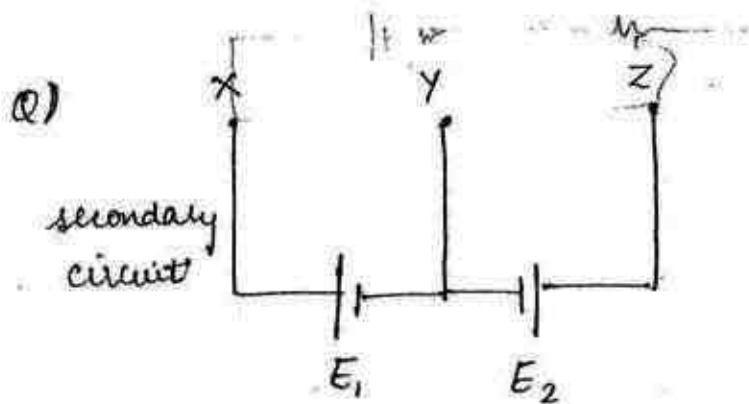
$$\frac{\phi_{\min}}{\phi_{\max}} = \frac{R + R_w}{R + R_w + R_{\max}}$$



when voltage b/w x and y is balanced on a potentiometer than balancing length is 700 cm but if voltage b/w x and z is balanced on the same potentiometer, then balancing length is 500 cm. & find  $E_1/E_2$

$$E_1 = \phi l_1$$

$$E_1 = \phi 700 \text{ --- (i)}$$

$$(E_1 - E_2) = \phi 500 \text{ --- (ii)}$$


from (i) and (ii)

$$\frac{E_1}{E_1 - E_2} = \frac{7}{5}$$

$$\therefore \frac{E_1}{E} = \frac{7}{9}$$

\* during experiment  $\phi$  remains unchanged  
 so we should not change setting of rheostat

Q1

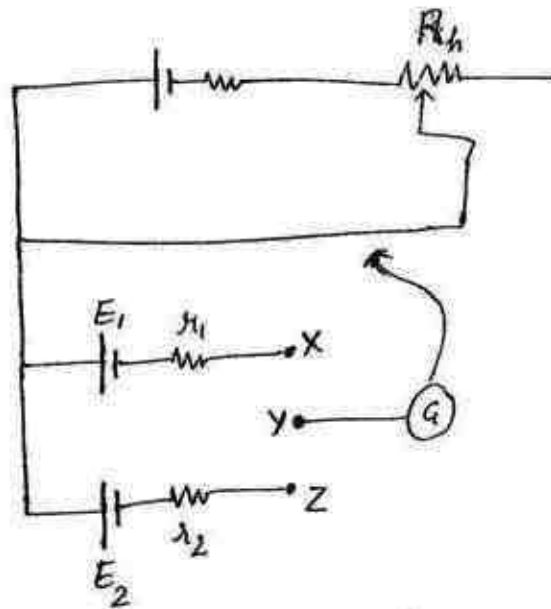

Comparison of  
 EMF of 2 cells

Why X and Y are short circuited, then balance length is  $l_1$ , now X and Y are disconnected and Y and Z are short-circuited, then balance length is  $l_2$ . Find  $E_1/E_2$


$$E_1 = \phi l_1$$

$$E_2 = \phi l_2$$

$$\therefore \frac{E_1}{E_2} = \frac{l_1}{l_2}$$

$\therefore$  Rheostat is not changed

Q)

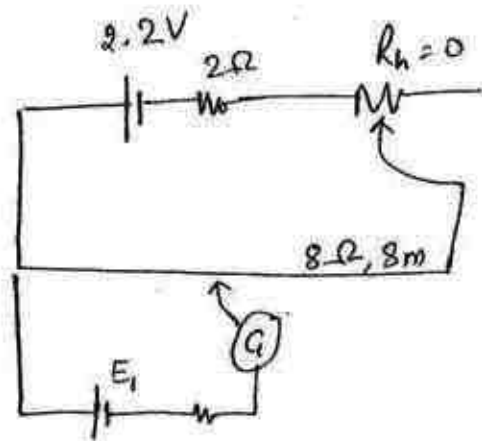


If balancing length of unknown cell is 5m.  
then find its emf

$$E_1 = \phi l$$

$$\therefore \phi = \frac{V_w}{L_w} = \frac{(I_w)R_w}{L_w} = \left( \frac{2.2}{2+0+8} \right) \times \frac{8}{8} = 0.22 \text{ V/m}$$

$$\therefore E_1 = 0.22 \times 5 = 1.1 \text{ V}$$

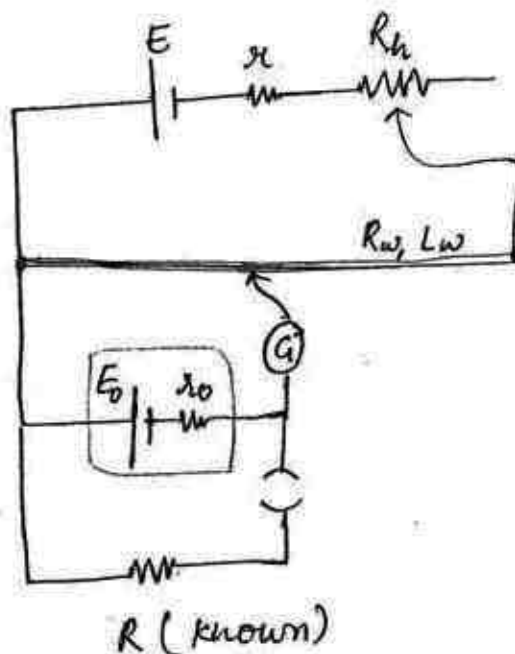★★★ To find internal resistance of a wire



In first part of experiment, key is kept open and emf,  $E_0$  is balanced on length  $l_0$  so

$$E_0 = \phi l_0 \quad \text{--- (1)}$$

In second part of the experiment, key is kept closed so there will be a current through the known resistance  $R$ .

Due to this current, potential of cell is its TPD and its balancing length is  $l_c$  ( $l_c < l_0$ )

and  $TPD = \phi l_c$

$$IR = \phi l_c \quad (\because TPD = IR)$$

Put value of  $I$

$$\left( \frac{E_0}{l_0 + R} \right) R = \phi l_c$$

$$\Rightarrow \left( \frac{\phi l_0}{l_0 + R} \right) R = \phi l_c$$


$$l_0 R = l_c l_0 + l_c R$$

$$R(l_0 - l_c) = l_c l_0$$

$$R_0 = \frac{R(l_0 - l_c)}{l_c}$$

★ Q) A cell is balanced on a potentiometer with and without short circuited by  $10\Omega$ . Its balancing length are  $100\text{ cm}$  and  $110\text{ cm}$  respectively. Find its internal resistance.
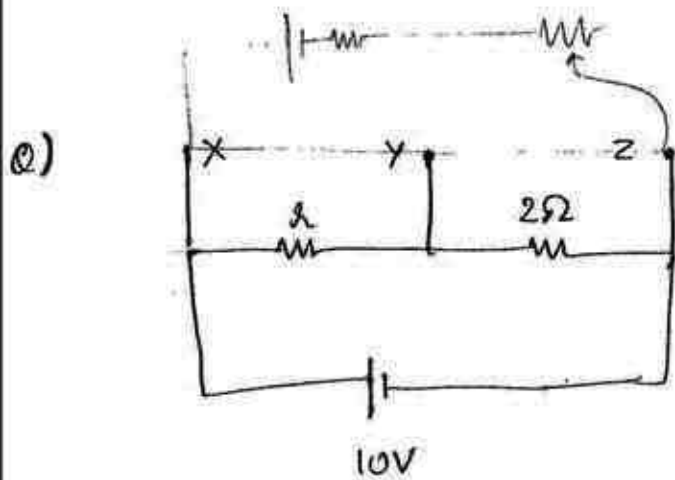
$$\therefore r_0 = \left( \frac{l_0 - l_c}{l_c} \right) R = \frac{110 - 100}{100} \times 10 = 1\Omega$$



} only secondary circuit is given.

Voltage b/w X and Y can be balanced on  $700\text{ cm}$  length of a potentiometer while voltage b/w X and Z can be balanced on  $900\text{ cm}$  length of same potentiometer. Find value of  $r$ .

$$V_1 = I r_1 = \phi (700) \text{--- (i)} \quad [ \because V = \phi l ]$$

$$V_1 + V_2 = I r_2 = \phi (900) \text{--- (ii)}$$

$$\frac{V_1}{V_1 + V_2} = \frac{700}{900}$$

$$9V_1 - 7V_1 = 7V_2$$

$$\therefore V_1 = 7V_2$$

$$7 \times 2 = 7V$$

$$7V$$

$$[ \because V_2 = 2 ]$$

XY balances on  $700$


YZ balances on  $200$

$\therefore 200\text{ cm}$  is shunted by  $2\Omega$  to balance

$\therefore 700\text{ cm}$  will be shunted by  $7\Omega$



Q)

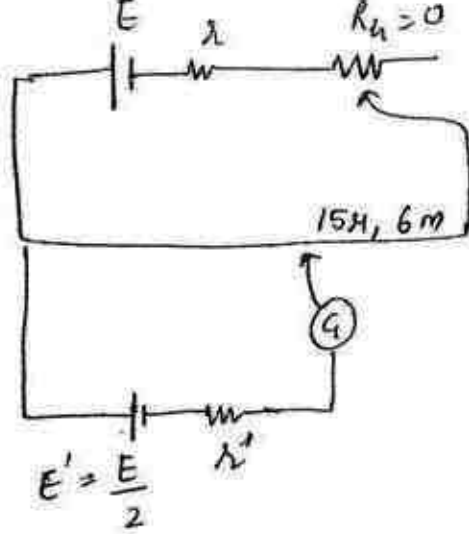

$$E' = \phi l$$

$$\frac{E}{2} = \left( \frac{E}{\lambda + 15\lambda + 0} \right) \frac{15\lambda}{6} \times l$$

$$\therefore 16\lambda = 5\lambda l$$

$$\therefore l = \frac{16}{5}$$

### Standardisation of Potentiometer:


To find potential gradient of a potentiometer with the help of a standard cell of known emf is called standardisation

$$E = \phi l \quad (E \text{ is known})$$

So,  $\phi = \frac{E}{l}$

$l$  has to be measured manually

Q)

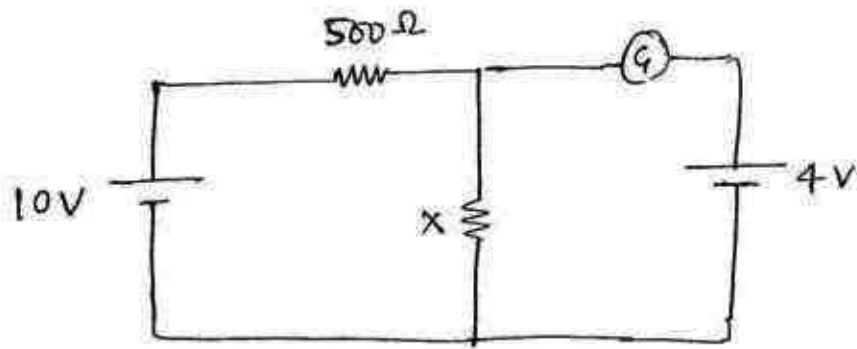

If deflection in  $G$  is 0 then find value of  $x$

$$I = \frac{V}{R}$$

$$= \left( \frac{10}{500 + x} \right)$$


$$V = IR \Rightarrow \left( \frac{10}{500 + x} \right) x = 4$$

$$\therefore 10x = 2000 + 4x$$

$$\therefore x = \frac{1000}{3} = 333.33 \Omega$$



Q)

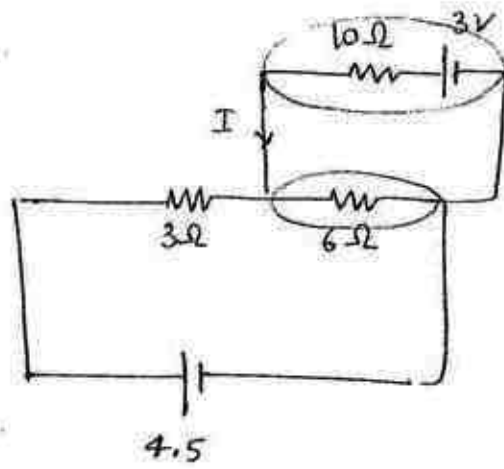

Calculate  $I = ?$

$$\therefore I = \frac{V}{R} = \frac{4.5}{6+3} = \frac{45}{90} = \frac{1}{2}$$


$$\therefore V = IR = \frac{1}{2} \times 6 = 3V$$

$\therefore$  both the wires have same potential

$\therefore$  no current will flow in  $6\Omega$  resistance

$$\therefore \boxed{I = 0}$$

# Colour code :

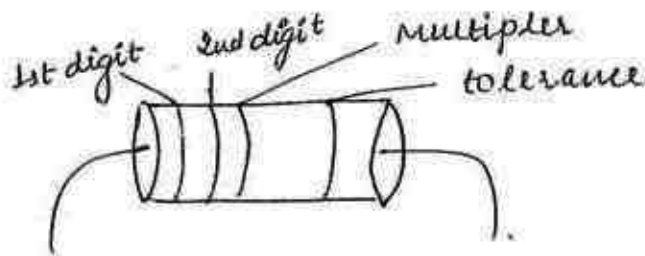

B	→	0	(Black)
B	→	1	(Brown)
R	→	2	(Red)
O	→	3	( <del>orange</del> orange)
Y	→	4	(Yellow)
G	→	5	(green)
B	→	6	(blue)
V	→	7	(violet)
G	→	8	(grey)
W	→	9	(white)


Memory tips: <sup>66</sup>

BBROY great  
 Britain very  
 good wife

gold  $\left\{ \begin{array}{l} \text{III} = 10^{-1} \\ \text{IV} = \pm 5\% \end{array} \right.$

silver  $\left\{ \begin{array}{l} \text{III} = 10^{-2} \\ \text{IV} = \pm 10\% \end{array} \right.$

IV (no colour)  $\Rightarrow \pm 20\%$

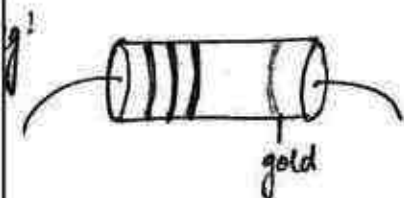


$(53 \times 10^6 \pm 5\%) \Omega$

Q) 2 bulb  $B_1$  (25W - 220V) and  $B_2$  (100W - 220V) are connected in series across a supply of 440V. Calculate voltage on each bulb and which bulb is more likely to fuse

$$R_1 = \frac{V_1^2}{P_1} = \frac{(22 \times 10)^2}{25} = (22)^2 \times 4$$
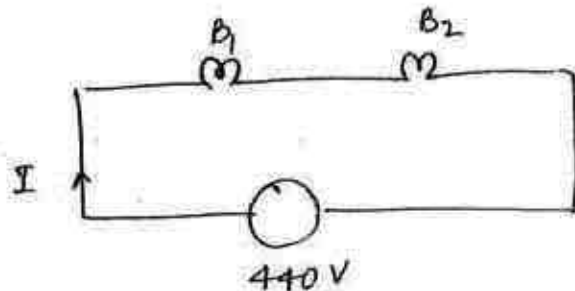
$$R_2 = \frac{V_2^2}{P_2} = \frac{(22 \times 10)^2}{100} = (22)^2$$



$$I = \frac{V_{net}}{R_{net}} = \frac{440}{22^2(4+1)} = \frac{440}{5 \times 22^2}$$

$$V_1 = I R_1 = \frac{440}{5 \times 22^2} \times 22^2 \times 4 \Rightarrow 352 \text{ V}$$

$$V_2 = I R_2 = \frac{440}{5 \times 22^2} \times 22^2 \Rightarrow 88 \text{ V}$$

OR  $\Rightarrow (440 - 352 = 88 \text{ V})$


$\therefore B_1$  is more likely to fuse

$\because$  it requires 220V of voltage but it is being supplied with 352V

Q)  $B_1$  (60W - 200V) and  $B_2$  (100W - 200V) and this combination is connected across a supply of 200V <sup>in series</sup>. Calculate total power generated

$$\therefore R_1 = \frac{V_1^2}{P_1} = \frac{200 \times 200}{60} = \frac{2000}{3}$$
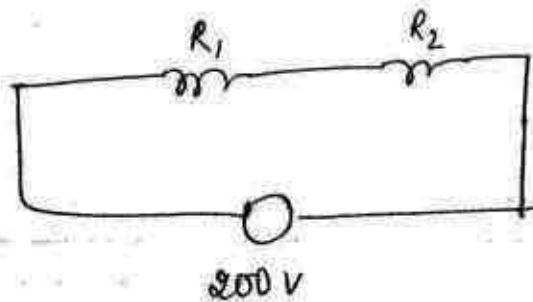
$$R_2 = \frac{V_2^2}{P_2} = \frac{200 \times 200}{100} = 400$$



$$\therefore I_{net} = \frac{V_{net}}{R_{net}} = \frac{200}{R_1 + R_2}$$

$$= \frac{200}{\frac{2000}{3} + 400} = \frac{200 \times 3}{3200} = \frac{3}{16}$$

$$P = VI = 200 \times \frac{3}{16} = \frac{75}{2} = \boxed{37.5 \text{ W}}$$

$$\therefore V_1 = IR_1 = \frac{3}{16} \times \frac{2000}{3} = 125 \text{ V}$$


$$V_2 = IR_2 = \frac{3}{16} \times 400 = \cancel{82.5 \text{ V}} \cdot 75 \text{ V}$$

$\therefore$  None of the bulbs will fuse

Q)  $B_1$  (60W - 200V) and  $B_2$  (60W - 200V) and this combination is connected across a supply of 200V. Calculate total power generated

$$R_1 = \frac{V_1^2}{P_1} = \frac{200 \times 200}{60} = \frac{2000}{3}$$
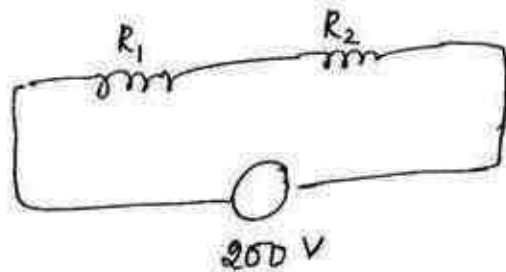
$$R_2 = \frac{V_2^2}{P_2} = \frac{200 \times 200}{60} = \frac{2000}{3}$$



$$\begin{aligned} \therefore I_{net} &= \frac{V_{net}}{R_{net}} = \frac{200}{\frac{2000}{3} + \frac{2000}{3}} \\ &= \frac{200 \times 3}{2 \times 2000} = \frac{3}{20} \end{aligned}$$

$$\therefore P = VI = 200 \times \frac{3}{20} = \boxed{30W}$$

$$\therefore V_1 = IR_1 = \frac{3}{20} \times \frac{2000}{3} = 100V$$

$$V_2 = IR_2 = \frac{3}{20} \times \frac{2000}{3} = 100V \text{ OR}$$

$$V_2 = V - V_1 = 200 - 100 = 100V$$

Power :

$$\frac{1}{P_s} = \frac{1}{P_1} + \frac{1}{P_2} \quad (\text{series})$$

$$P_p = P_1 + P_2 \quad (\text{Parallel})$$